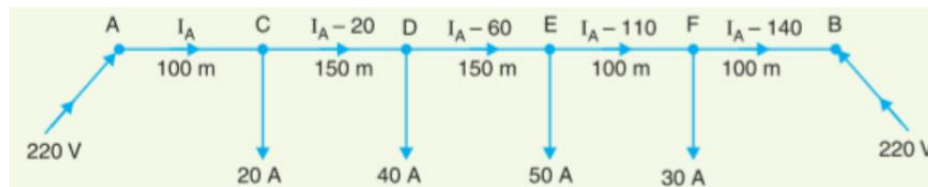


LTspice simulations for DC distribution systems

LTspice simulator, you can download it for free: <https://www.analog.com/en/design-center/design-tools-and-calculators/ltspice-simulator.html>

Task: Find currents in the arms AC, CD, DE, EF, and FB in the DC distribution system with two voltage sources at both ends. The main equation is $V_B = V_A - V_{AB}$, where V_{AB} is the total voltage drop along AB for the chosen current directions. We initially assume that all currents flow in a specific positive direction along the line. However, in the calculation process, it's possible that some currents might appear negative, indicating their actual direction is opposite to the originally chosen direction.



Resistance of 1 m length of distributor

$$= 2 \times \frac{1.7 \times 10^{-6} \times 100}{1} = 3.4 \times 10^{-4} \Omega$$

Resistance of section AC, $R_{AC} = (3.4 \times 10^{-4}) \times 100 = 0.034 \Omega$

Resistance of section CD, $R_{CD} = (3.4 \times 10^{-4}) \times 150 = 0.051 \Omega$

Resistance of section DE, $R_{DE} = (3.4 \times 10^{-4}) \times 150 = 0.051 \Omega$

Resistance of section EF, $R_{EF} = (3.4 \times 10^{-4}) \times 100 = 0.034 \Omega$

Resistance of section FB, $R_{FB} = (3.4 \times 10^{-4}) \times 100 = 0.034 \Omega$

The loads' utility is defined based on consumption currents rather than resistances. Resistances serve to characterize losses in the distribution system between nodes from which the load currents are drawn.

Analytical solution:

or

$$\text{Voltage at } B = \text{Voltage at } A - \text{Drop over length } AB$$

$$V_B = V_A - [I_A R_{AC} + (I_A - 20) R_{CD} + (I_A - 60) R_{DE} + (I_A - 110) R_{EF} + (I_A - 140) R_{FB}]$$

or

$$220 = 220 - [0.034 I_A + 0.051 (I_A - 20) + 0.051 (I_A - 60) + 0.034 (I_A - 110) + 0.034 (I_A - 140)]$$


$$= 220 - [0.204 I_A - 12.58]$$

or


$$0.204 I_A = 12.58$$

∴


$$I_A = 12.58 / 0.204 = 61.7 \text{ A}$$



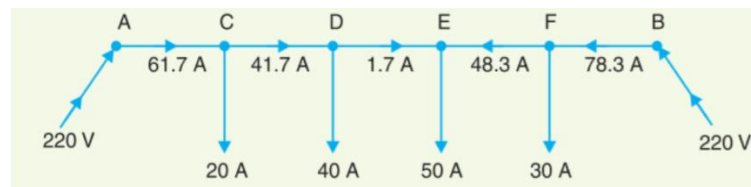


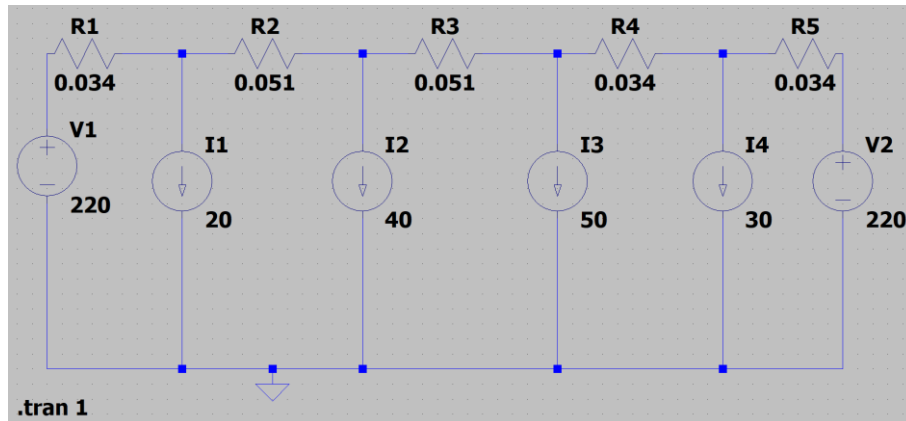In LTspice, constant current sources are utilized instead of resistors to represent the consumption characteristics (file “[DC_Both_Ends_1.asc](#)” in the folder “LTspice_DC_distribution_systems”):



Double left-click on R1, R2, R3, R4, or R5 to show the current simulation (straight line). A single left-click will retain the previous reading of the current. Simulation time doesn't factor in since we're dealing with constant voltages and currents. We've set it to 1 second (**.tran 1**). For some reason, LTspice displays currents with opposite signs. Please consider this when verifying your analytical solutions:



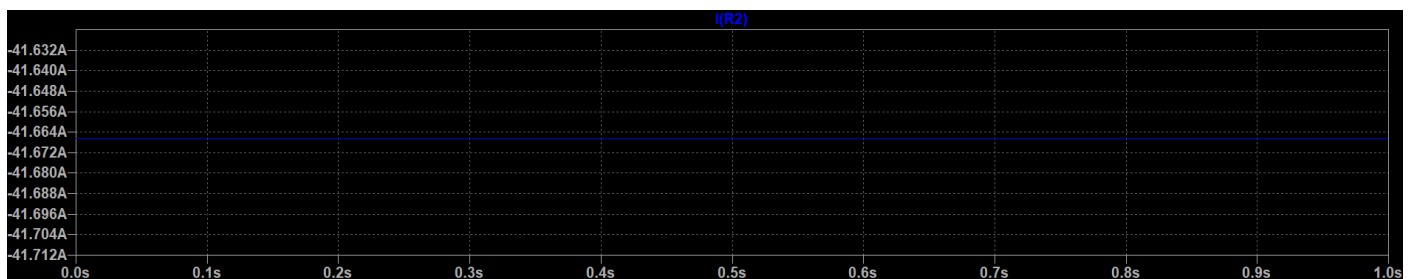



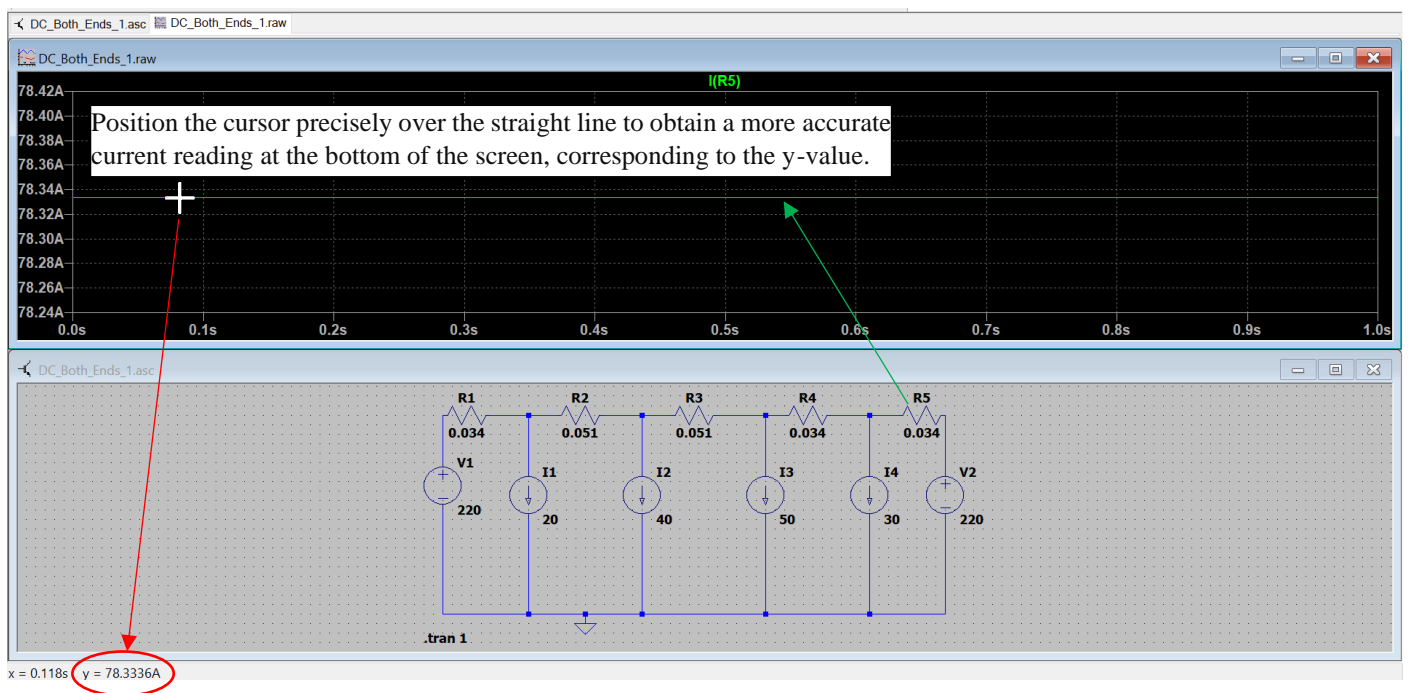
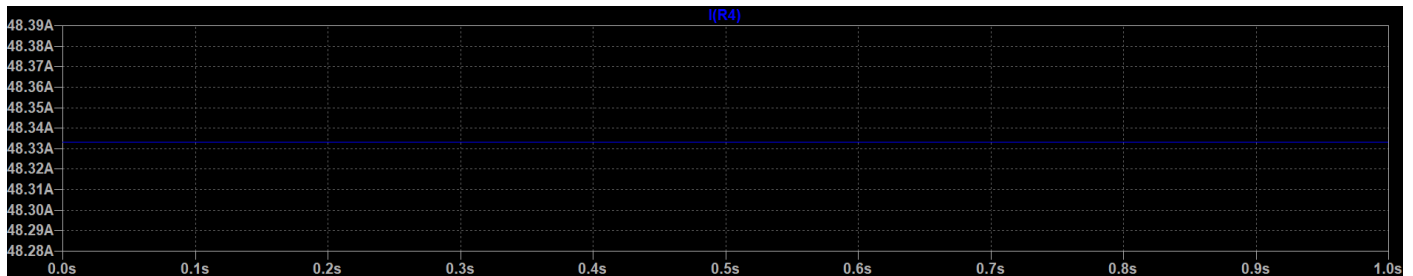
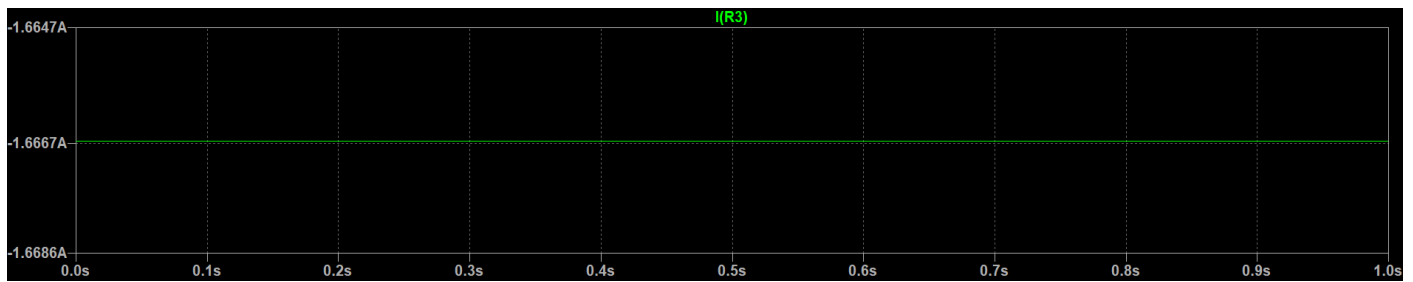


In LTspice, the current direction displayed might seem opposite to what one might expect based on the [conventional assumption](#). This occurrence can sometimes puzzle users who are new to the software or those who haven't encountered this behaviour before. It's more about how LTspice represents current flow rather than adhering strictly to the conventional assumption. If you've just discovered this feature and find it

unexpected or puzzling, that's completely normal. Learning about these software-specific behaviours often takes time and experimentation.

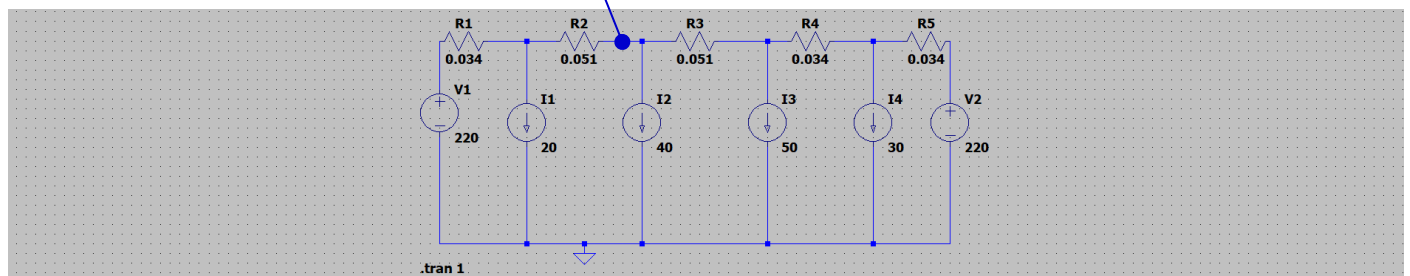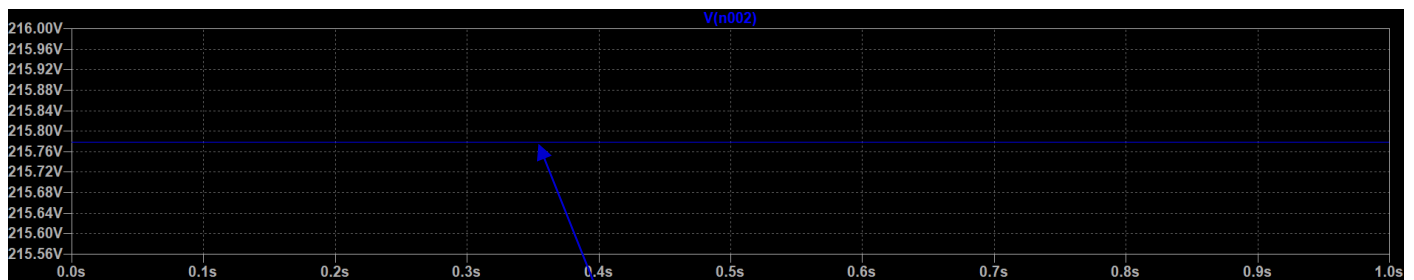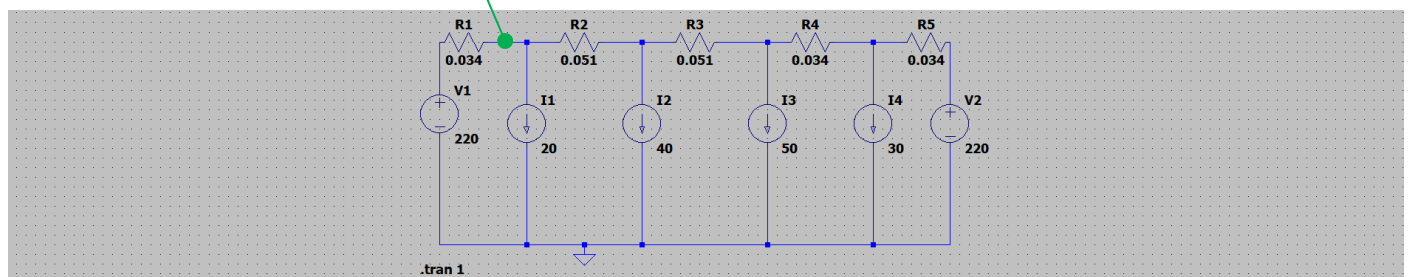To measure the voltage at a specific test point, left-click the cursor on the wire passing through that point:



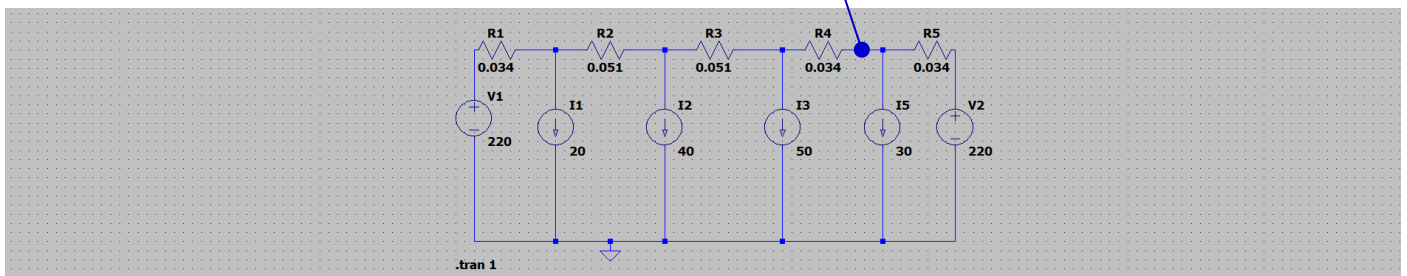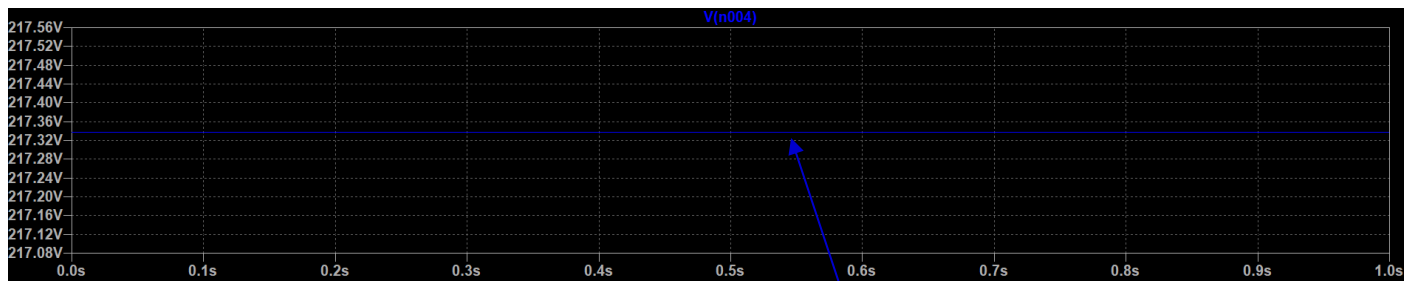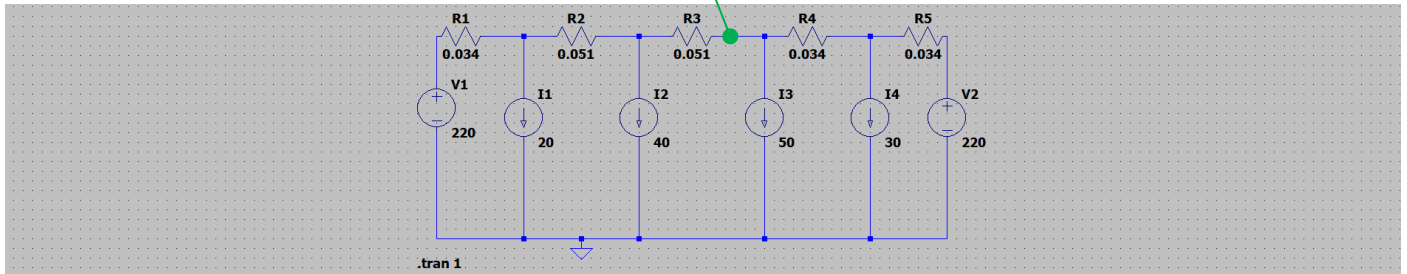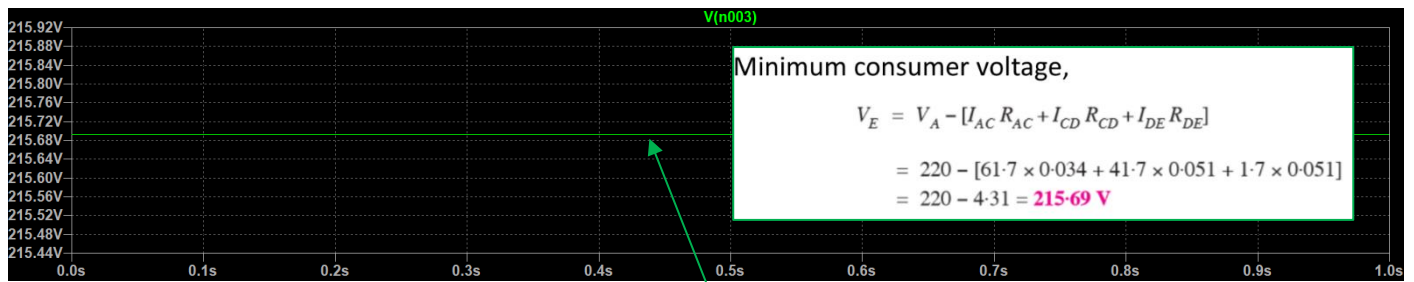

Task:

A 2-wire d.c. distributor AB is fed from both ends. At feeding point A, the voltage is maintained at 230 V and at B 235 V. The total length of the distributor is 200 metres and loads are tapped off as follows:

25 A at 50 metres from A ; 50 A at 75 metres from A

30 A at 100 metres from A ; 40 A at 150 metres from A

The resistance per kilometre of one conductor is 0.3Ω .

Calculate: (i) currents in various sections of the distributor (ii) minimum voltage and the point at which it occurs

Solution:

Resistance of 1000 m length of distributor (both wires)

$$= 2 \times 0.3 = 0.6 \Omega$$

Resistance of section AC, $R_{AC} = 0.6 \times 50/1000 = 0.03 \Omega$

Resistance of section CD, $R_{CD} = 0.6 \times 25/1000 = 0.015 \Omega$

Resistance of section DE, $R_{DE} = 0.6 \times 25/1000 = 0.015 \Omega$

Resistance of section EF, $R_{EF} = 0.6 \times 50/1000 = 0.03 \Omega$

Resistance of section FB, $R_{FB} = 0.6 \times 50/1000 = 0.03 \Omega$

Voltage at B = Voltage at A – Drop over AB

$$V_B = V_A - [I_A R_{AC} + (I_A - 25) R_{CD} + (I_A - 75) R_{DE} + (I_A - 105) R_{EF} + (I_A - 145) R_{FB}]$$

$$235 = 230 - [0.03 I_A + 0.015 (I_A - 25) + 0.015 (I_A - 75) + 0.03 (I_A - 105) + 0.03 (I_A - 145)]$$

$$235 = 230 - [0.12 I_A - 9]$$

$$\therefore I_A = \frac{239 - 235}{0.12} = 33.34 \text{ A}$$


(i) \therefore Current in section AC, $I_{AC} = I_A = 33.34 \text{ A}$
 Current in section CD, $I_{CD} = I_A - 25 = 33.34 - 25 = 8.34 \text{ A}$

Current in section DE, $I_{DE} = I_A - 75 = 33.34 - 75 = -41.66 \text{ A}$ from D to E
 $= 41.66 \text{ A}$ from E to D

Current in section EF, $I_{EF} = I_A - 105 = 33.34 - 105 = -71.66 \text{ A}$ from E to F
 $= 71.66 \text{ A}$ from F to E


Current in section $FB, I_{FB} = I_A - 145 = 33.34 - 145 = -111.66 \text{ A}$ from F to B
 $= 111.66 \text{ A}$ from B to F

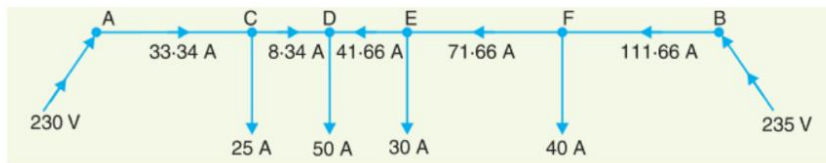(ii) The actual distribution of currents in the various sections of the distributor







$$\begin{aligned} \text{Voltage at } D, V_D &= V_A - [I_{AC} R_{AC} + I_{CD} R_{CD}] \\ &= 230 - [33.34 \times 0.03 + 8.34 \times 0.015] \\ &= 230 - 1.125 = 228.875 \text{ V} \end{aligned}$$


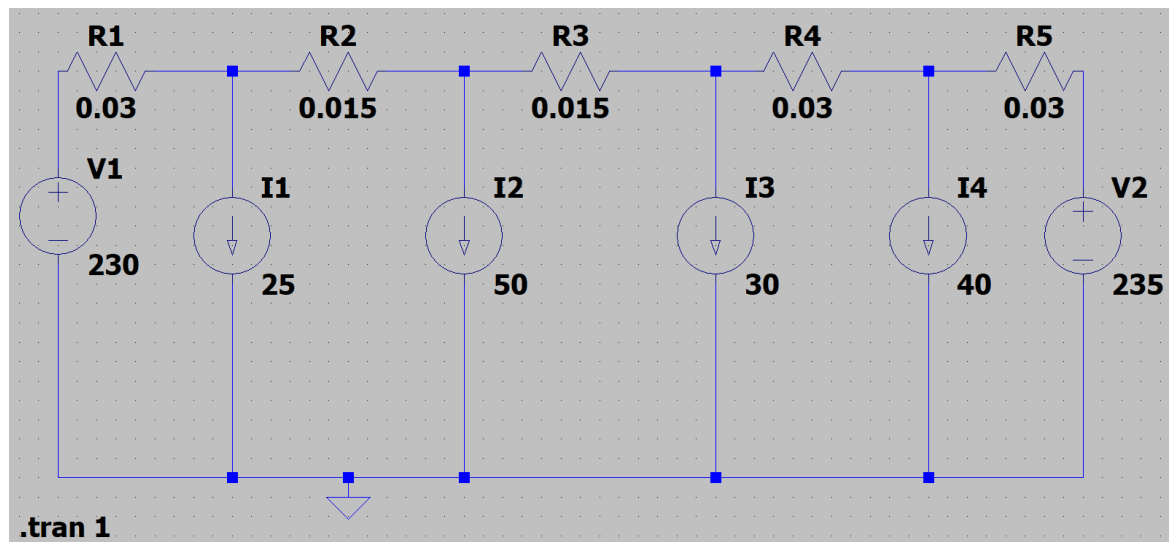
File “DC_Both_Ends_2.asc” in the folder “LTspice_DC_distribution_systems”:




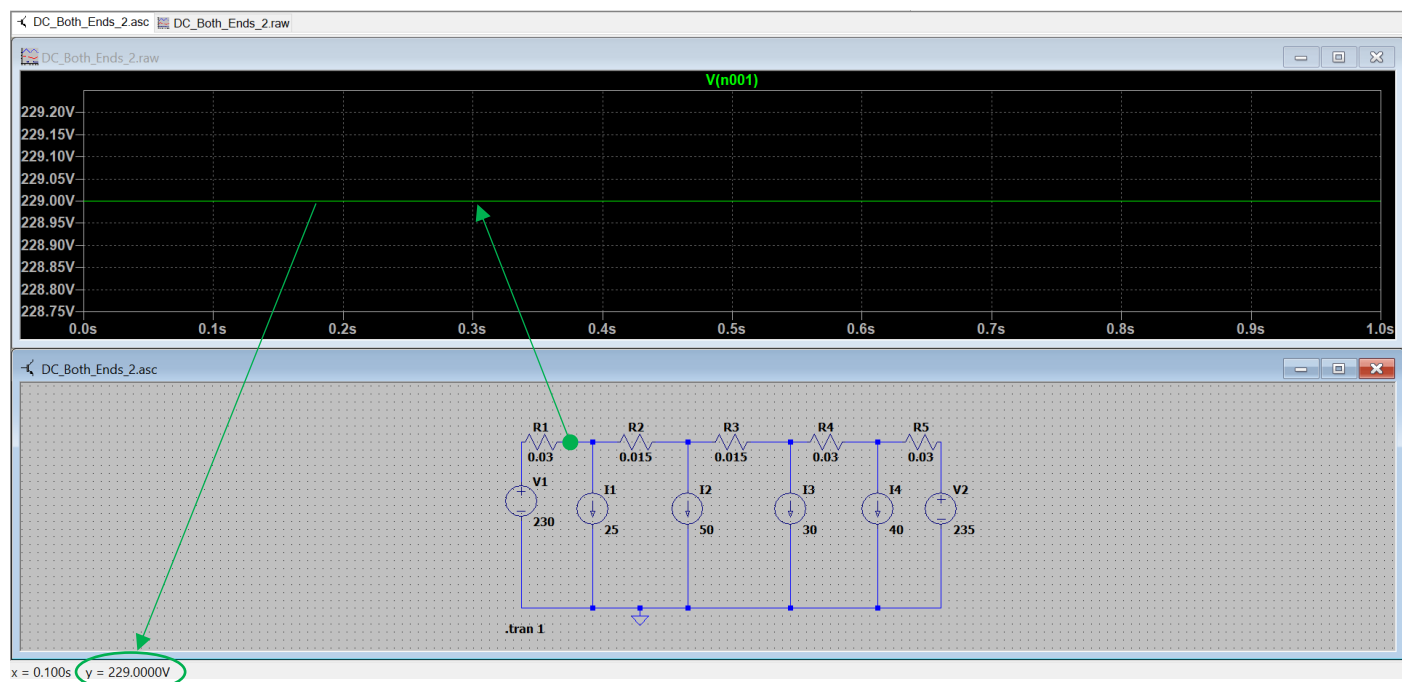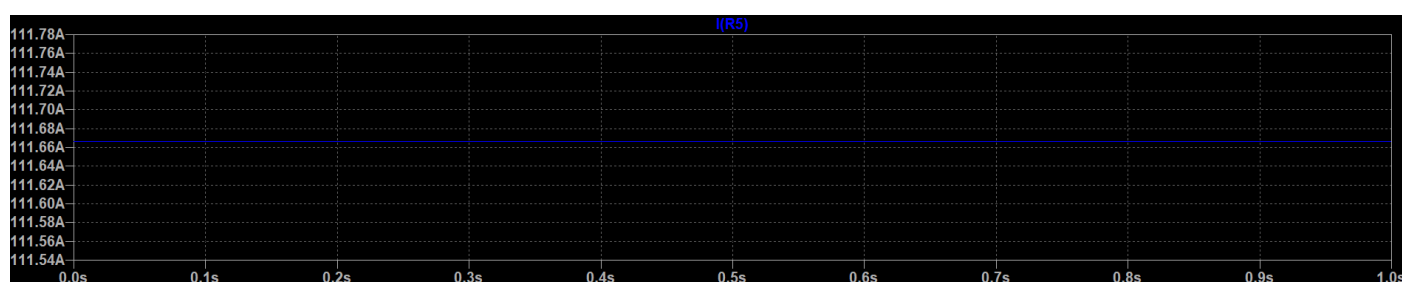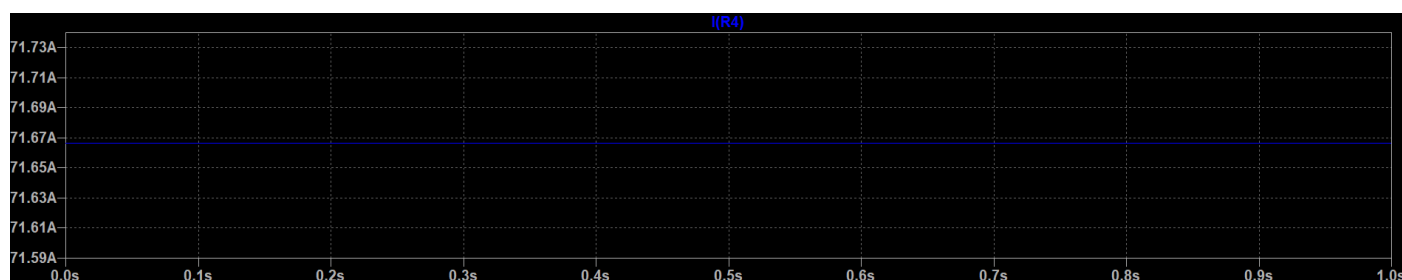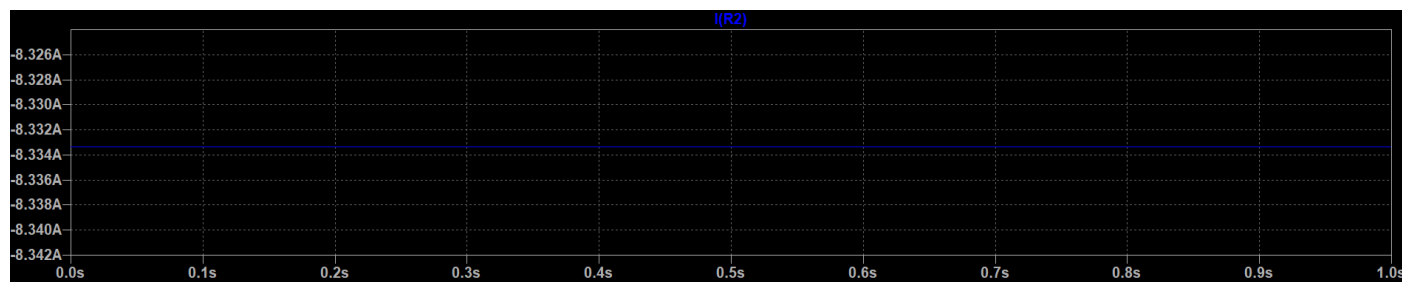Simulation of the currents through R1-R5. Keep in mind the sign convention in LTspice when interpreting the results. The software might represent values with different signs than expected due to the [usual convention](#):






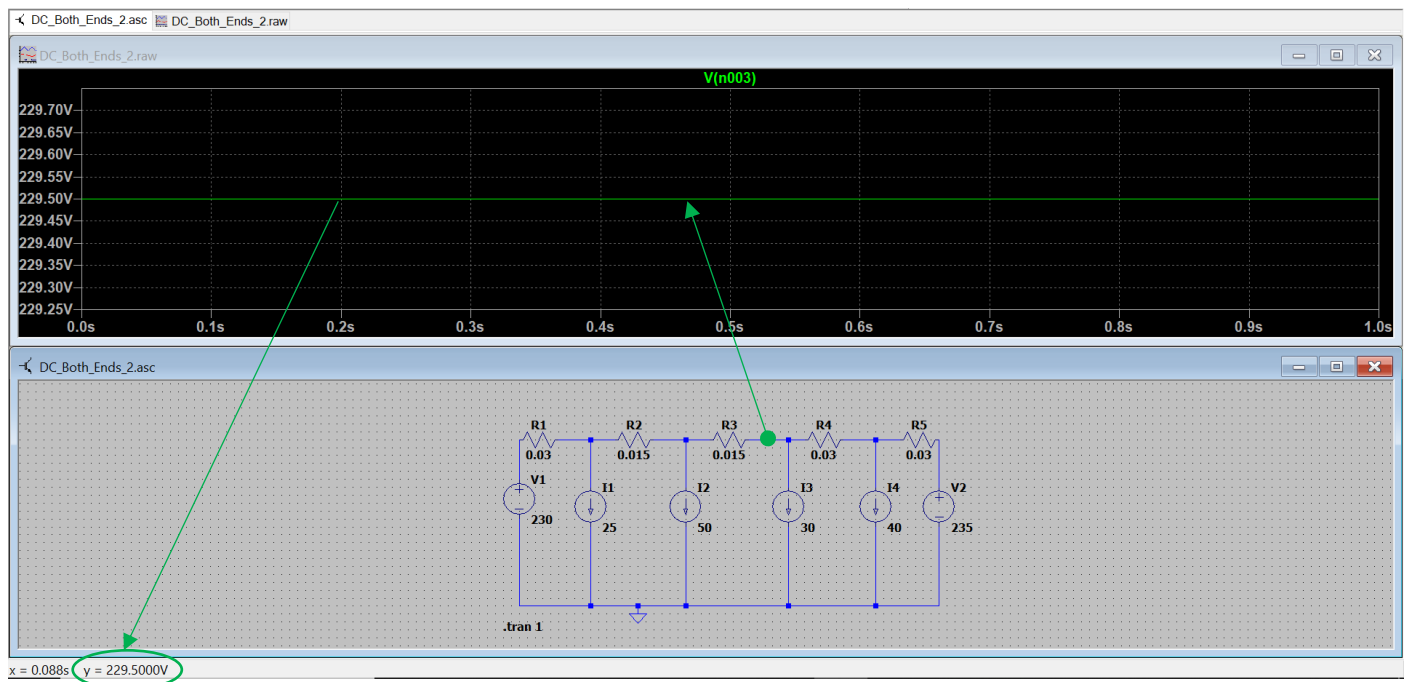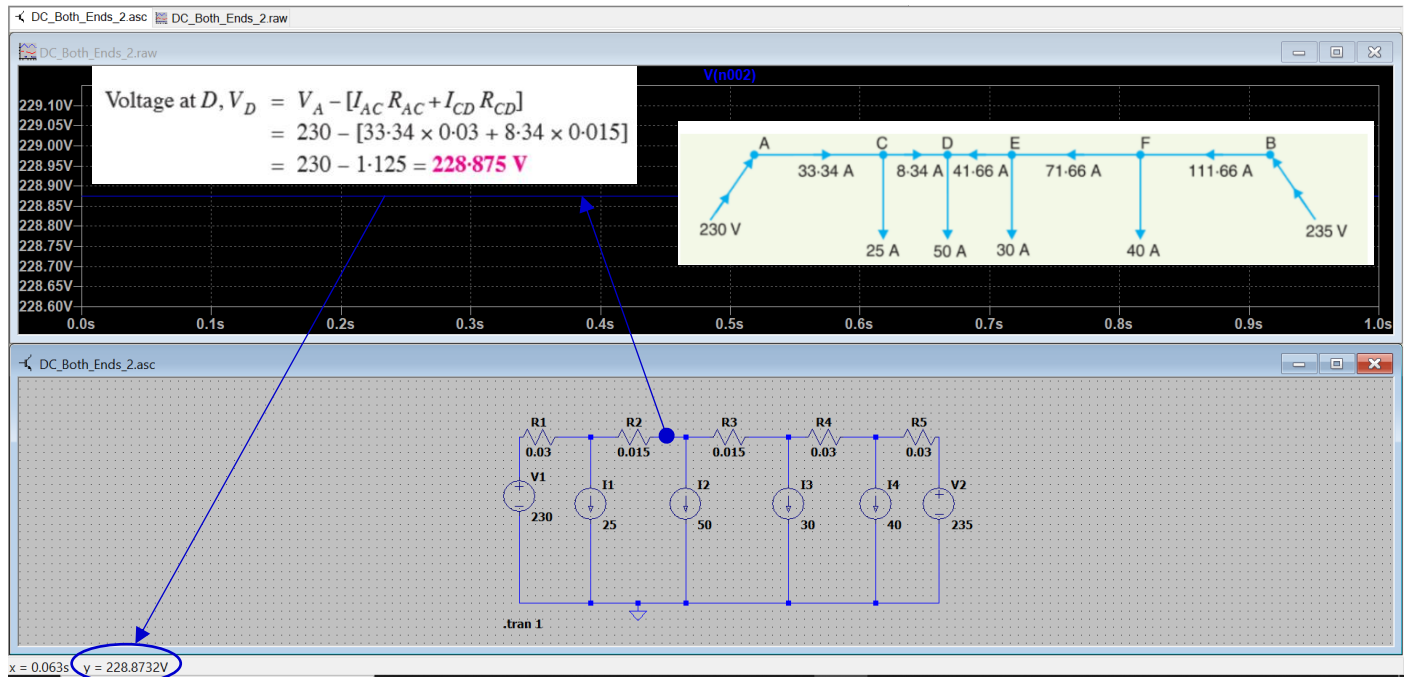

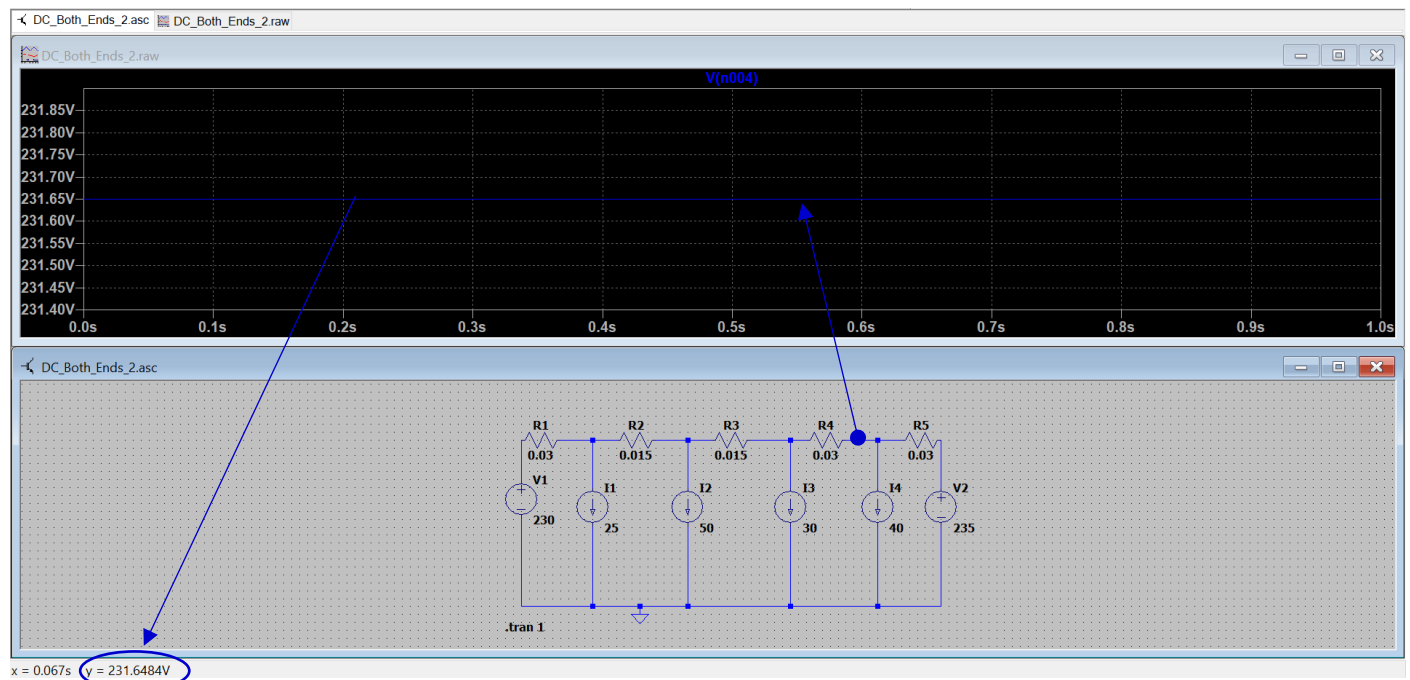

Task:

A 2-wire d.c. distributor cable AB is 2 km long and supplies loads of 100A, 150A, 200A and 50A situated 500 m, 1000 m, 1600 m and 2000 m from the feeding point A. Each conductor has a resistance of 0.01Ω per 1000 m. Calculate the p.d. at each load point if a p.d. of 300 V is maintained at point A.

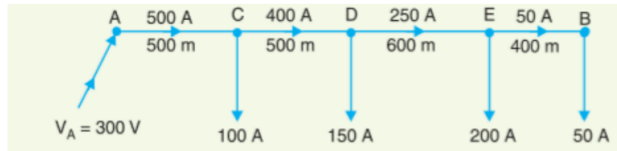**Solution:**

The fundamental condition for a distribution system fed at one end is that the incoming current equals the sum of all currents branching across the loads.

Resistance per 1000 m of distributor = $2 \times 0.01 = 0.02 \Omega$

Resistance of section AC, $R_{AC} = 0.02 \times 500/1000 = 0.01 \Omega$

Resistance of section CD, $R_{CD} = 0.02 \times 500/1000 = 0.01 \Omega$

Resistance of section DE, $R_{DE} = 0.02 \times 600/1000 = 0.012 \Omega$

Resistance of section EB, $R_{EB} = 0.02 \times 400/1000 = 0.008 \Omega$

Referring to Fig. 13.6, the currents in the various sections of the distributor are :

$$\begin{aligned} I_{EB} &= 50 \text{ A}; & I_{DE} &= 50 + 200 = 250 \text{ A} \\ I_{CD} &= 250 + 150 = 400 \text{ A}; & I_{AC} &= 400 + 100 = 500 \text{ A} \end{aligned}$$






$$\begin{aligned} \text{P.D. at load point C, } V_C &= \text{Voltage at A} - \text{Voltage drop in AC} \\ &= V_A - I_{AC} R_{AC} \\ &= 300 - 500 \times 0.01 = \mathbf{295 \text{ V}} \end{aligned}$$



$$\begin{aligned} \text{P.D. at load point D, } V_D &= V_C - I_{CD} R_{CD} \\ &= 295 - 400 \times 0.01 = \mathbf{291 \text{ V}} \end{aligned}$$



$$\begin{aligned} \text{P.D. at load point E, } V_E &= V_D - I_{DE} R_{DE} \\ &= 291 - 250 \times 0.012 = \mathbf{288 \text{ V}} \end{aligned}$$

$$\begin{aligned} \text{P.D. at load point B, } V_B &= V_E - I_{EB} R_{EB} \\ &= 288 - 50 \times 0.008 = \mathbf{287.6 \text{ V}} \end{aligned}$$

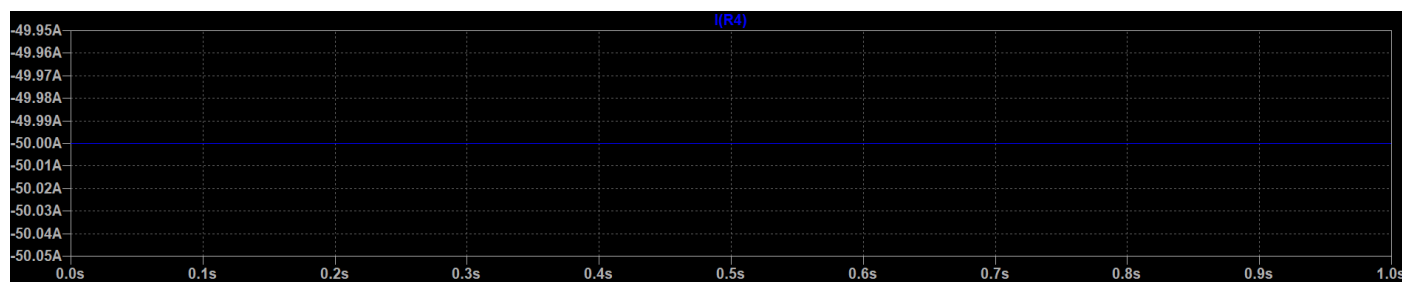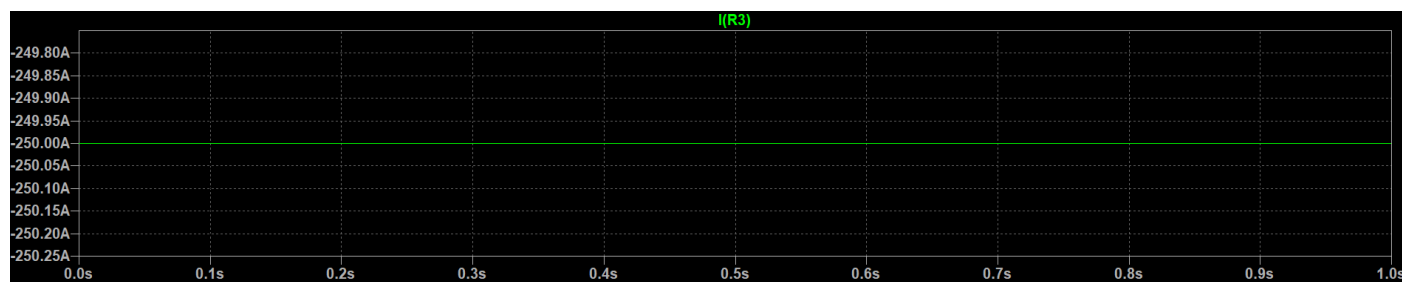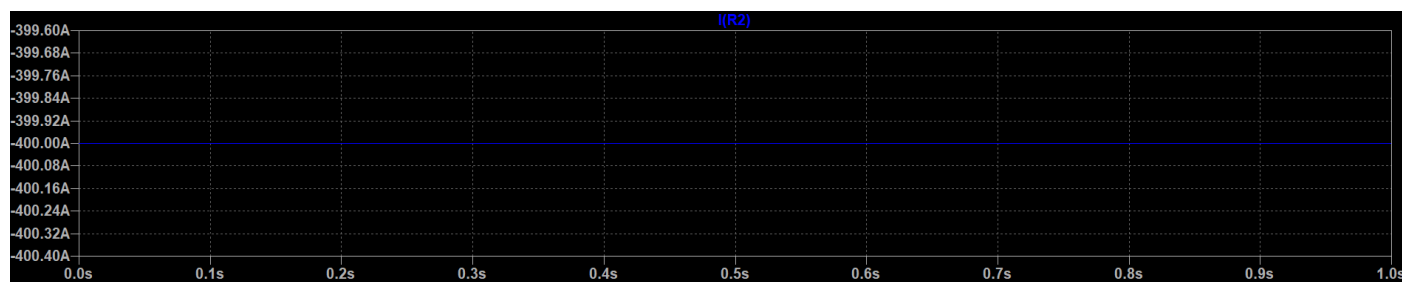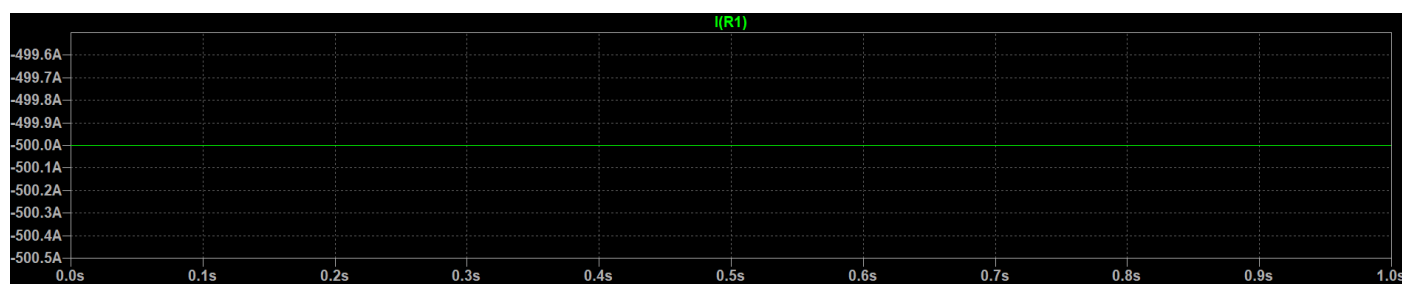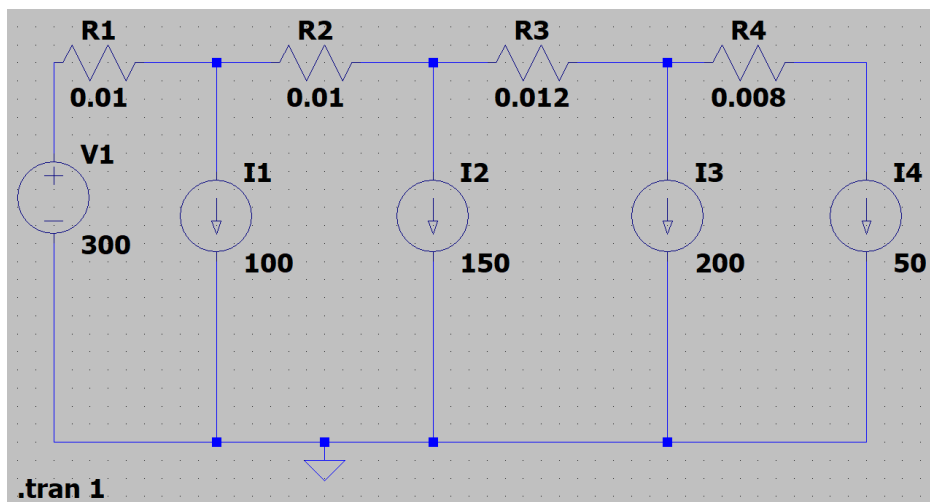(file “DC_Single_End.asc” in the folder “LTspice_DC_distribution_systems”)



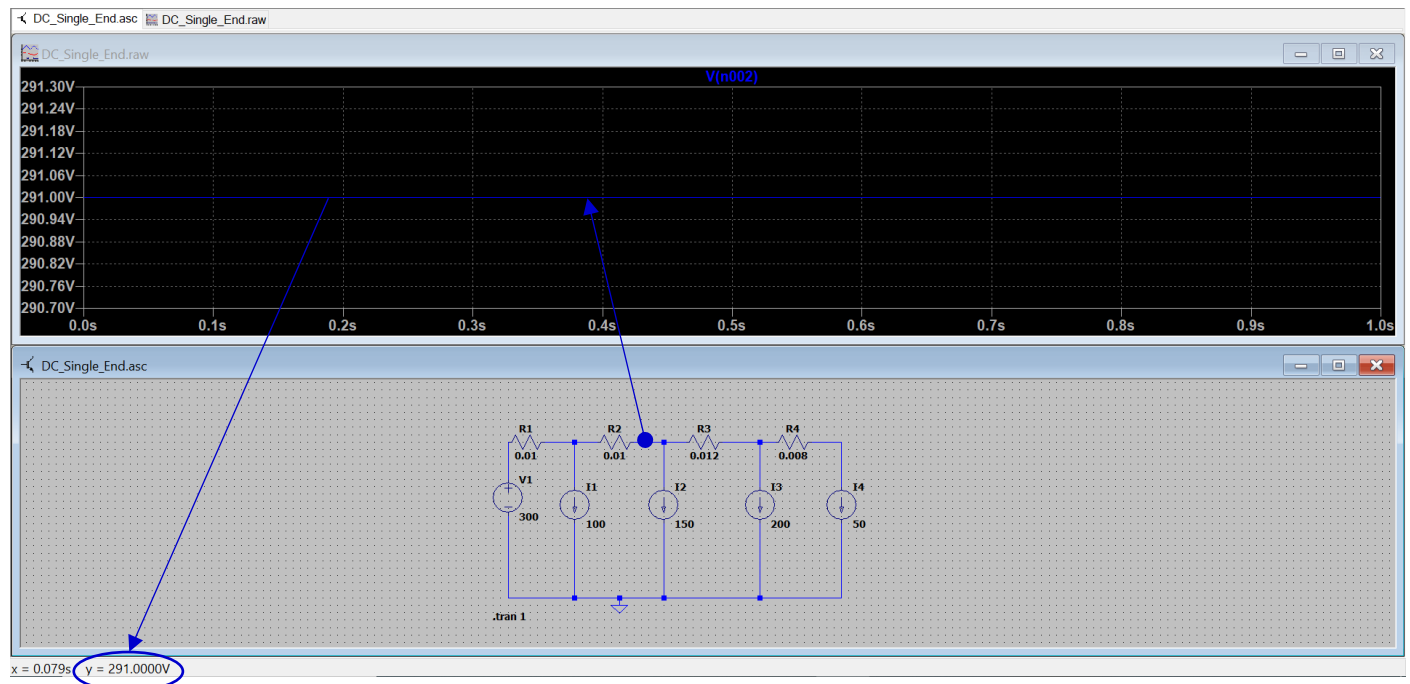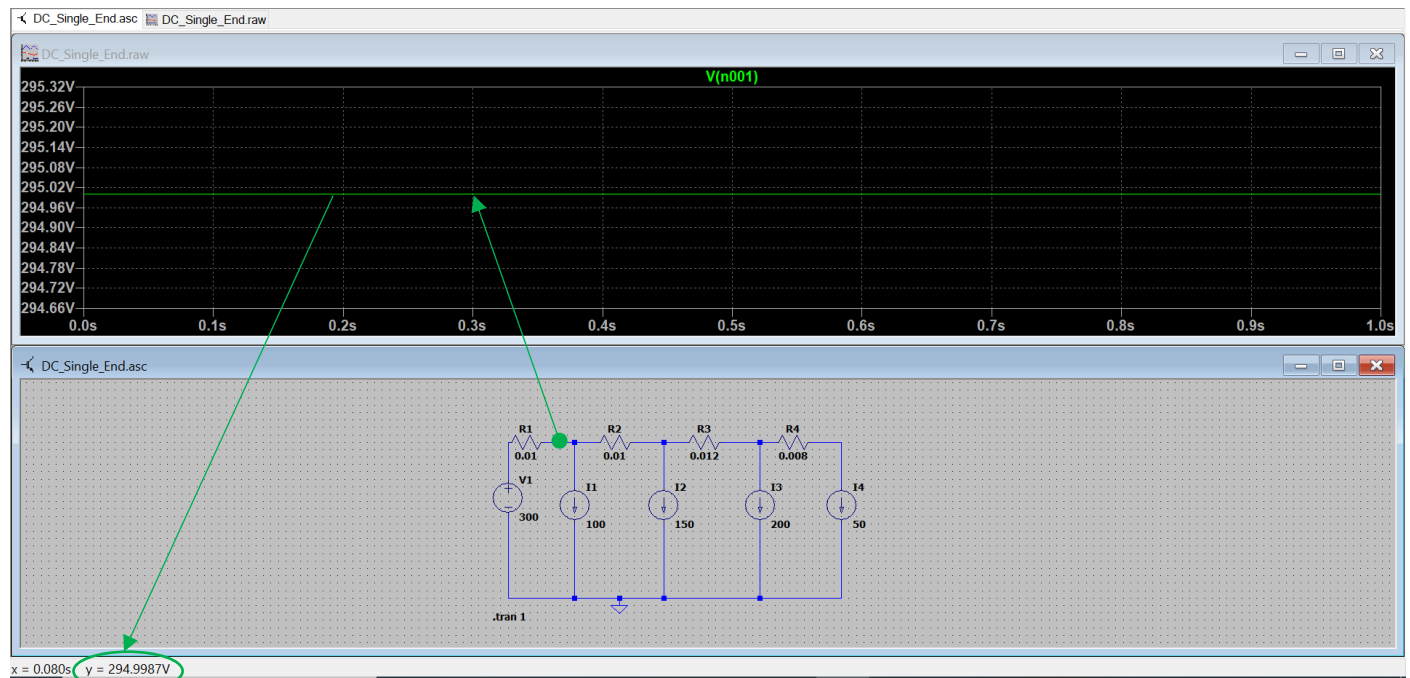

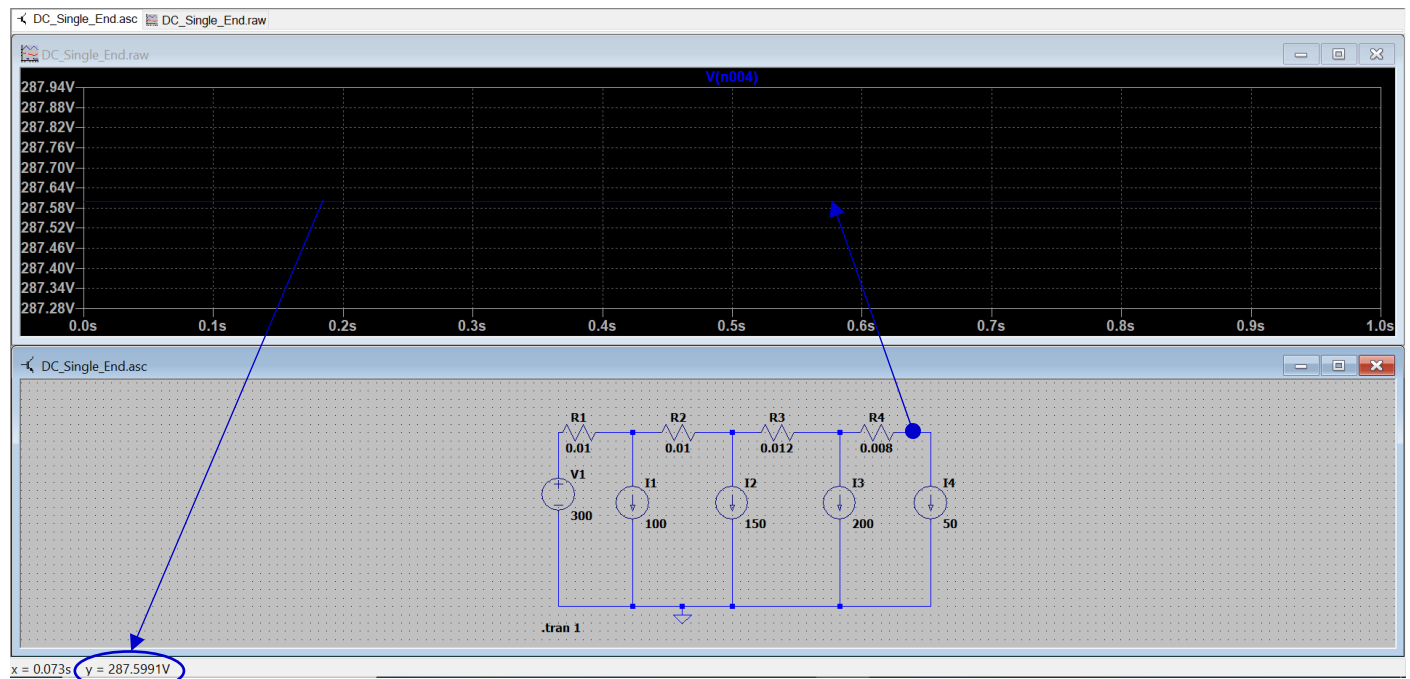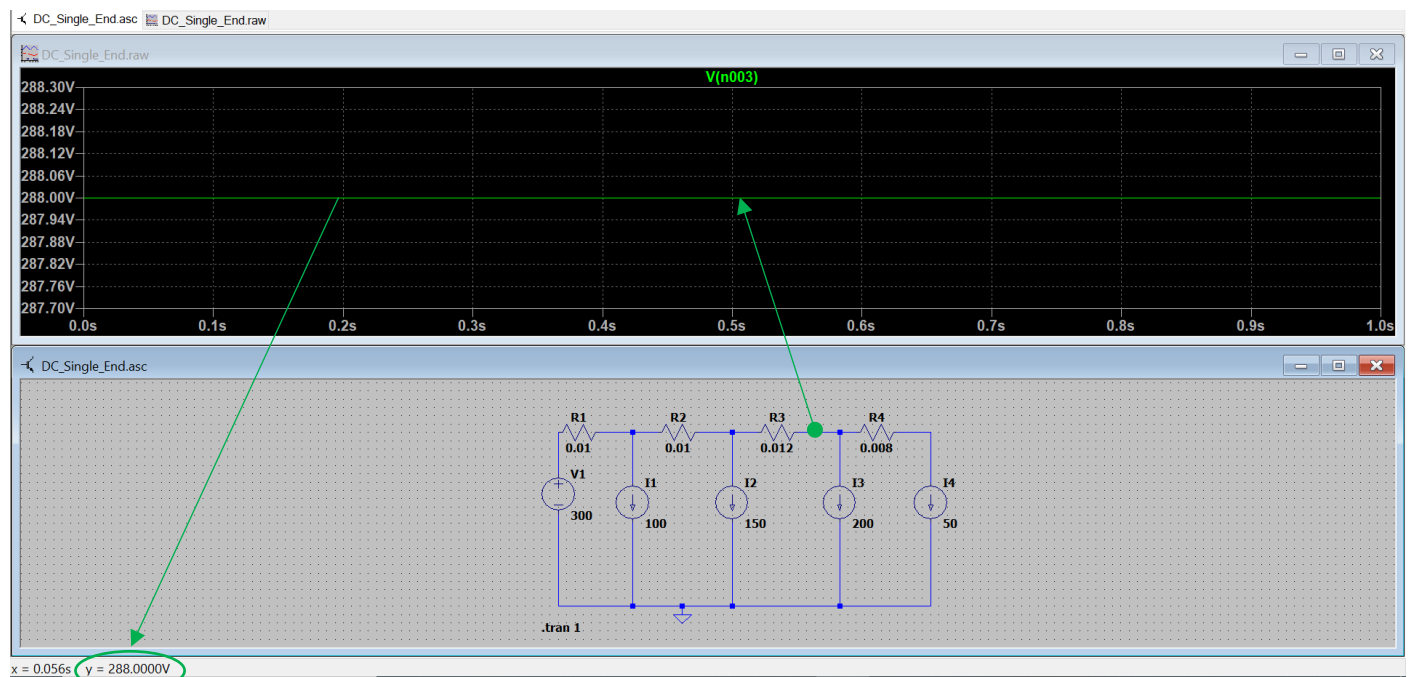

Task:

A 2-wire d.c. ring distributor is 300 m long and is fed with 240 V at point A. At point B, 150 m from A, a load of 120 A is taken and at C, 100 m in the opposite direction, a load of 80 A is taken. If the resistance per 100 m of single conductor is 0.03Ω , find : (i) current in each section of distributor (ii) voltage at points B and C .

Solution.


Resistance per 100 m of distributor

$$= 2 \times 0.03 = 0.06 \Omega$$


Resistance of section AB, $R_{AB} = 0.06 \times 150/100 = 0.09 \Omega$

Resistance of section BC, $R_{BC} = 0.06 \times 50/100 = 0.03 \Omega$

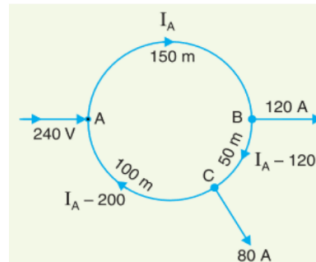Resistance of section CA, $R_{CA} = 0.06 \times 100/100 = 0.06 \Omega$



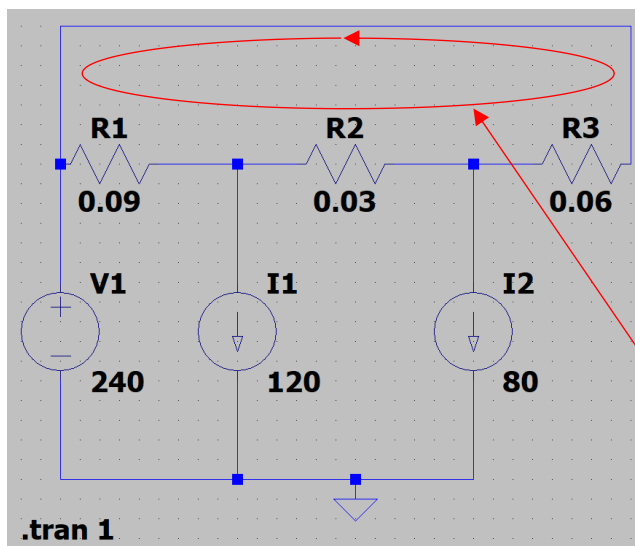(file “DC_Ring_1.asc” in the folder “LTspice_DC_distribution_systems”)



Let us assume that current I_A flows in section AB of the distributor. Then currents in sections BC and CA will be $(I_A - 120)$ and $(I_A - 200)$ respectively as shown in the Figure above.

According to Kirchhoff's voltage law, the voltage drop in the closed loop ABCA is zero i.e.


$$I_{AB} R_{AB} + I_{BC} R_{BC} + I_{CA} R_{CA} = 0$$

$$\text{or } 0.09 I_A + 0.03 (I_A - 120) + 0.06 (I_A - 200) = 0$$

$$\text{or } 0.18 I_A = 15.6$$

$$\therefore I_A = 15.6/0.18 = 86.67 \text{ A}$$

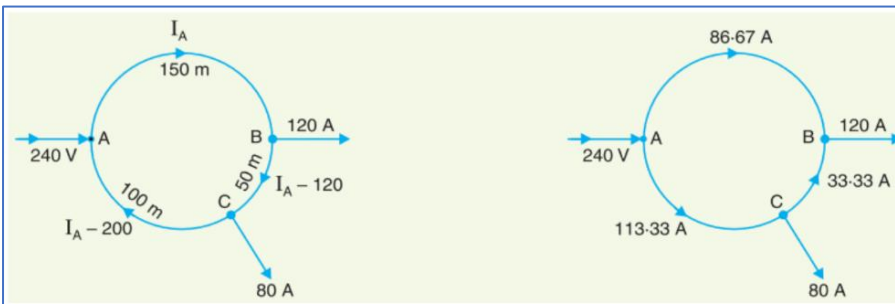The actual distribution of currents is as shown in Figure below from where it is seen that B is the point of minimum potential.






Current in section AB , $I_{AB} = I_A = 86.67 \text{ A}$ from A to B



Current in section BC , $I_{BC} = I_A - 120 = 86.67 - 120 = -33.33 \text{ A}$
 $= 33.33 \text{ A}$ from C to B

Current in section CA , $I_{CA} = I_A - 200 = 86.67 - 200 = -113.33 \text{ A}$
 $= 113.33 \text{ A}$ from A to C

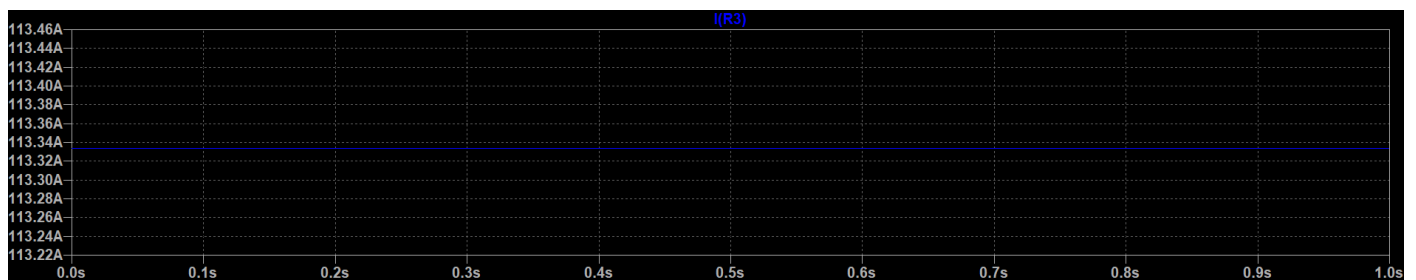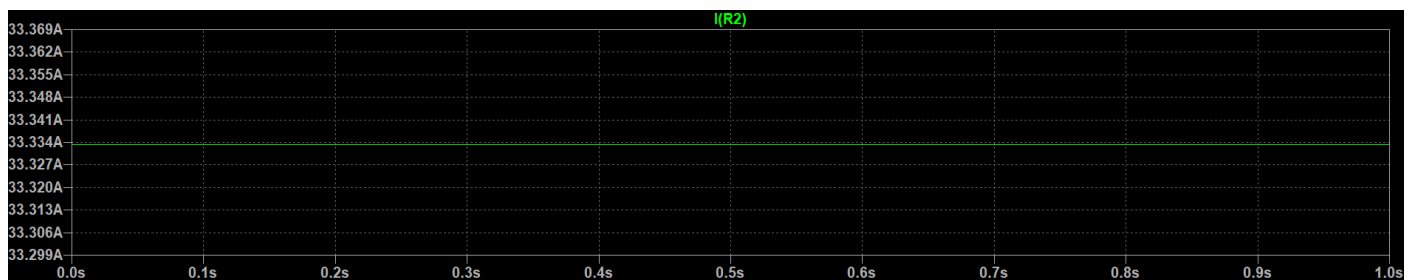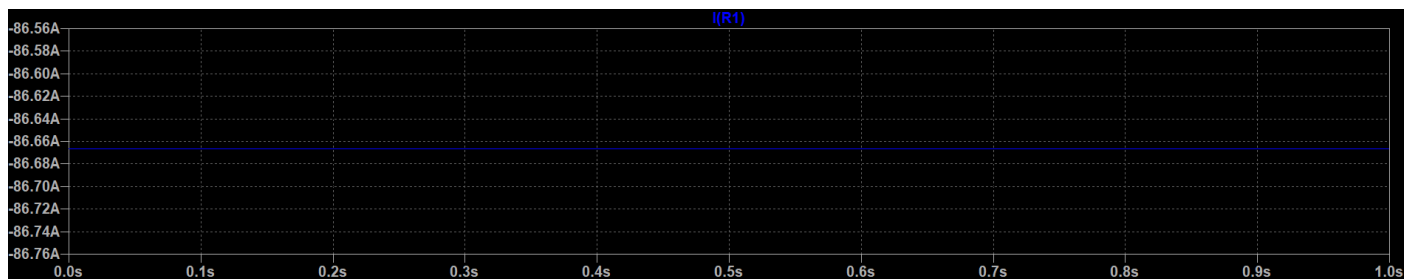(ii) Voltage at point B , $V_B = V_A - I_{AB} R_{AB} = 240 - 86.67 \times 0.09 = 232.2 \text{ V}$

Voltage at point C , $V_C = V_B + I_{BC} R_{BC}$
 $= 232.2 + 33.33 \times 0.03 = 233.2 \text{ V}$





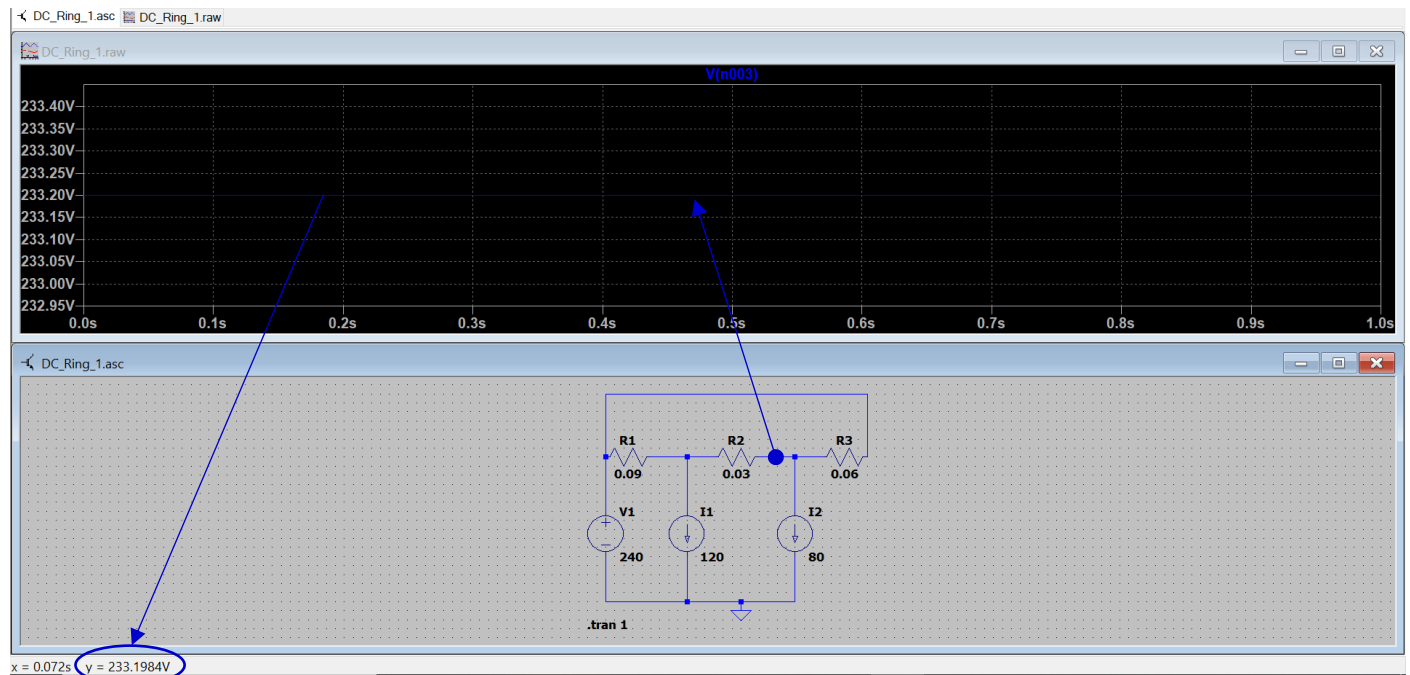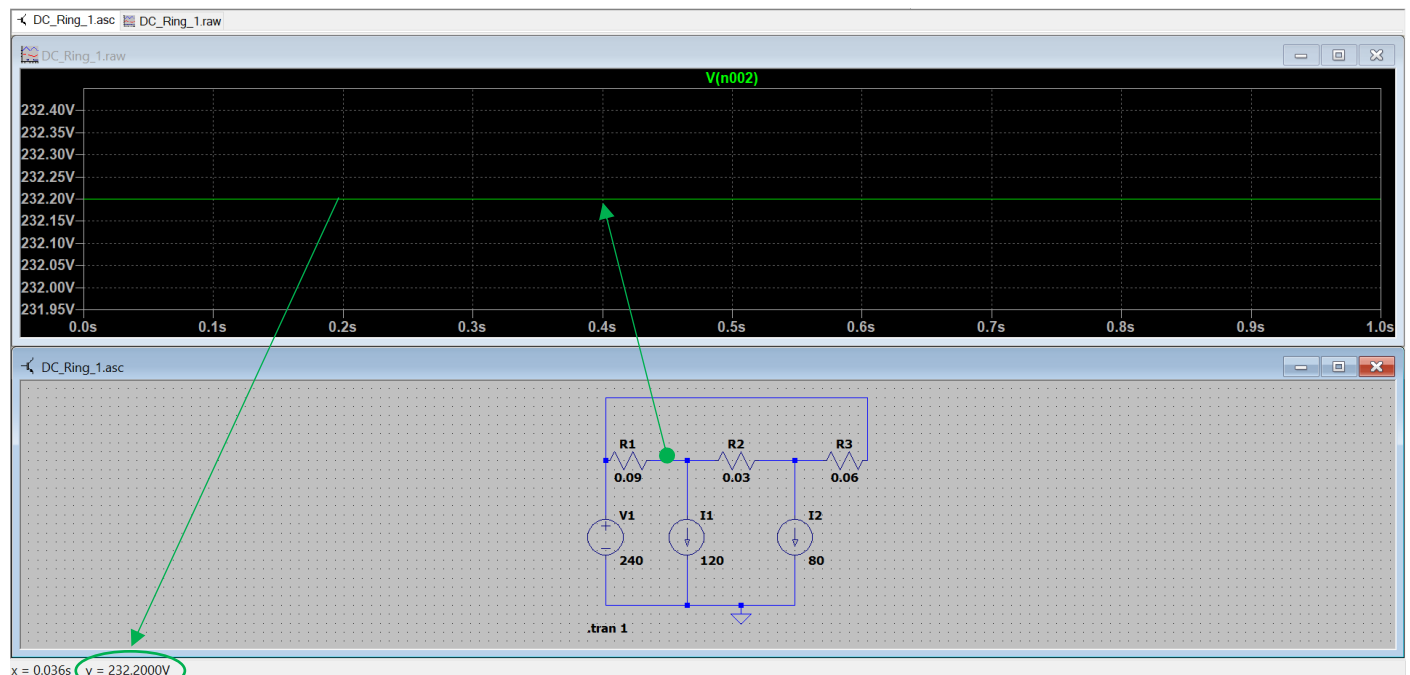


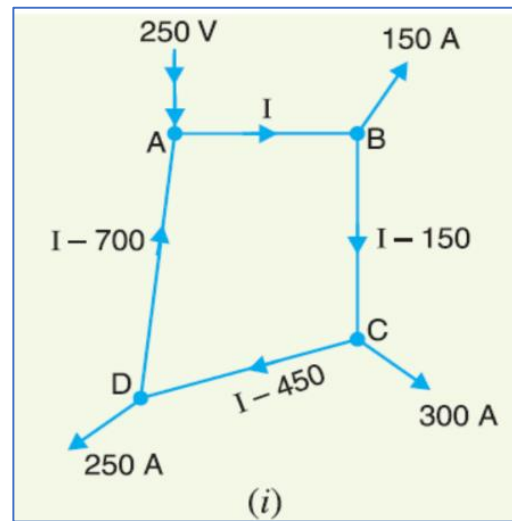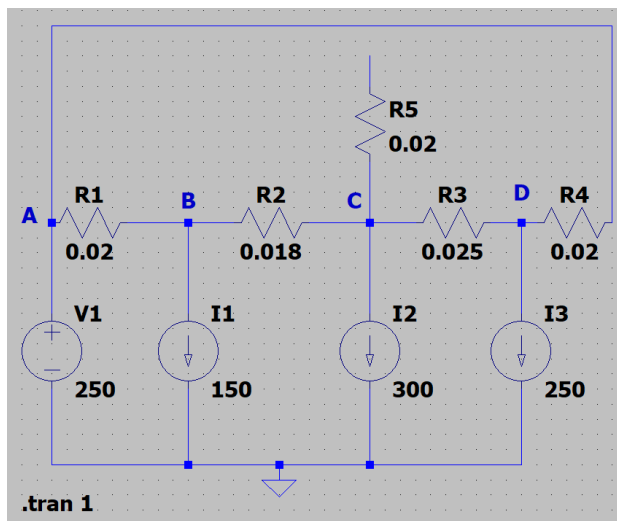Task:

A d.c. ring main ABCDA is fed from point A from a 250 V supply and the resistances (including both lead and return) of various sections are as follows : $AB = 0.02 \Omega$; $BC = 0.018 \Omega$; $CD = 0.025 \Omega$ and $DA = 0.02 \Omega$. The main supplies loads of 150 A at B ; 300 A at C and 250 A at D. Determine the voltage at each load point. If the points A and C are linked through an interconnector of resistance 0.02Ω , determine the new voltage at each load point.

(file “DC_Ring_2.asc” in the folder “LTspice_DC_distribution_systems”)



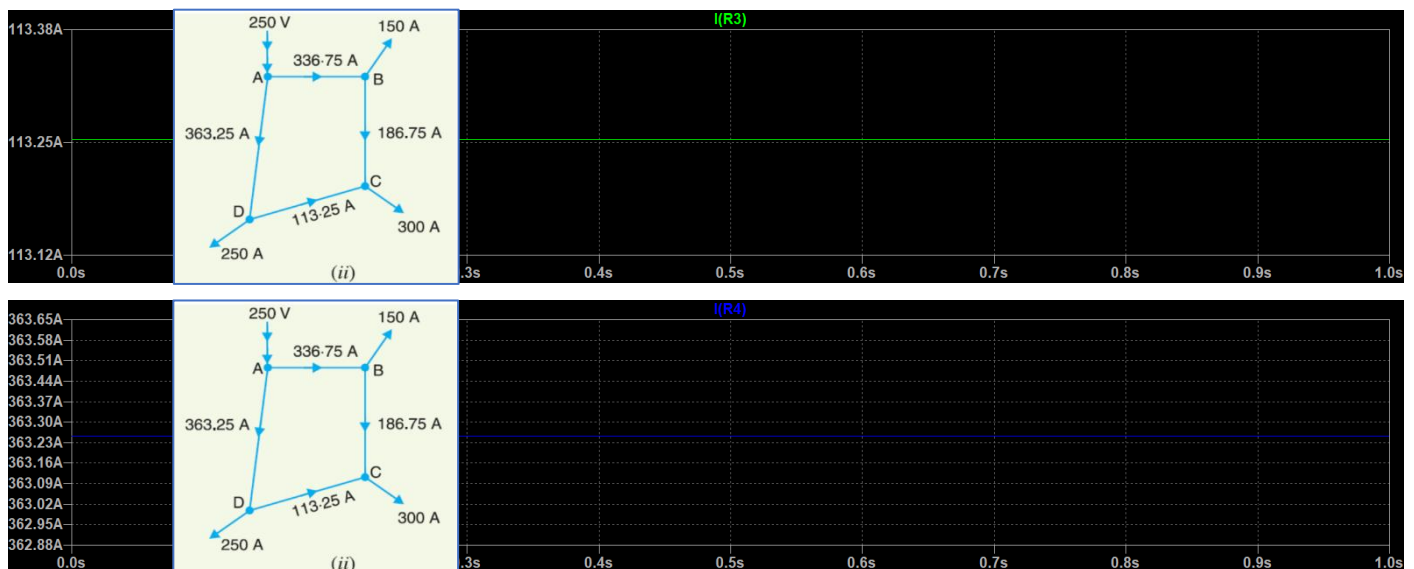

$$\text{Voltage drop in } AB = 336.75 \times 0.02 = 6.735 \text{ V}$$

$$\text{Voltage drop in } BC = 186.75 \times 0.018 = 3.361 \text{ V}$$


$$\text{Voltage drop in } CD = 113.25 \times 0.025 = 2.831 \text{ V}$$



$$\text{Voltage drop in } DA = 363.25 \times 0.02 = 7.265 \text{ V}$$





$$\text{Voltage at point } B = 250 - 6.735 = 243.265 \text{ V}$$


$$\text{Voltage at point } C = 243.265 - 3.361 = 239.904 \text{ V}$$
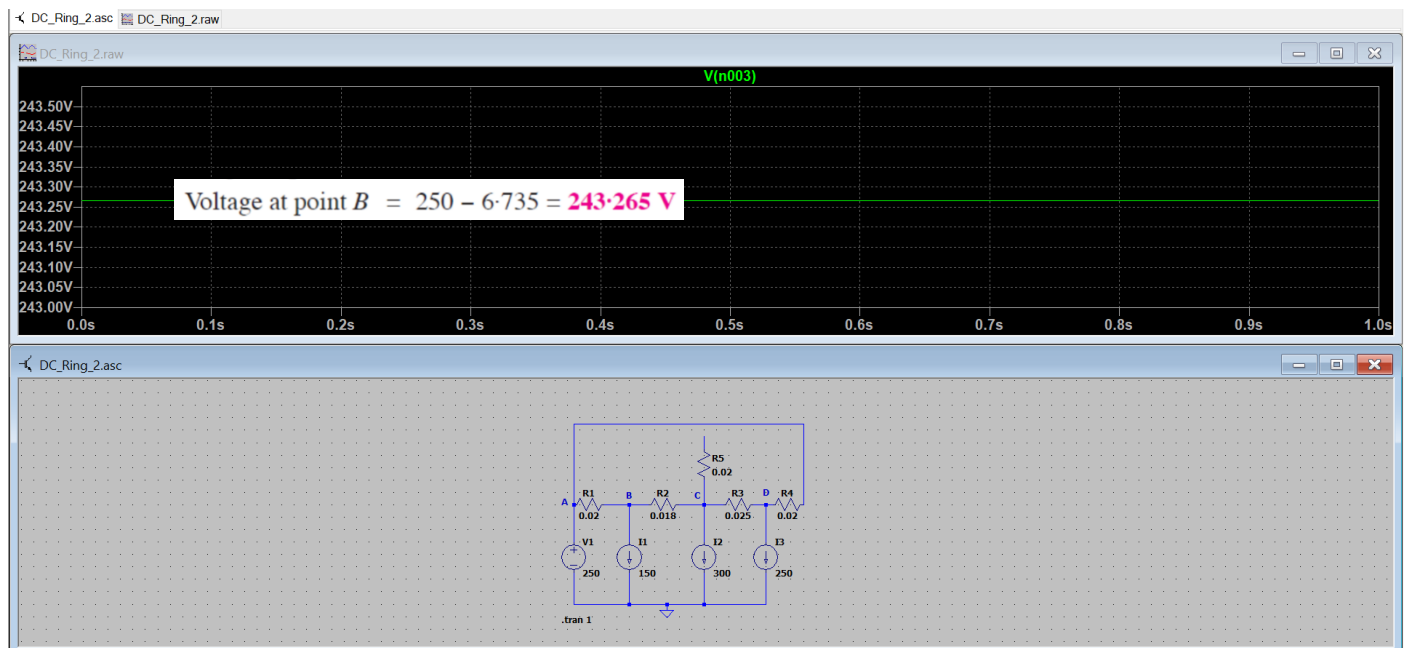
$$\text{Voltage at point } D = 239.904 + 2.831 = 242.735 \text{ V}$$





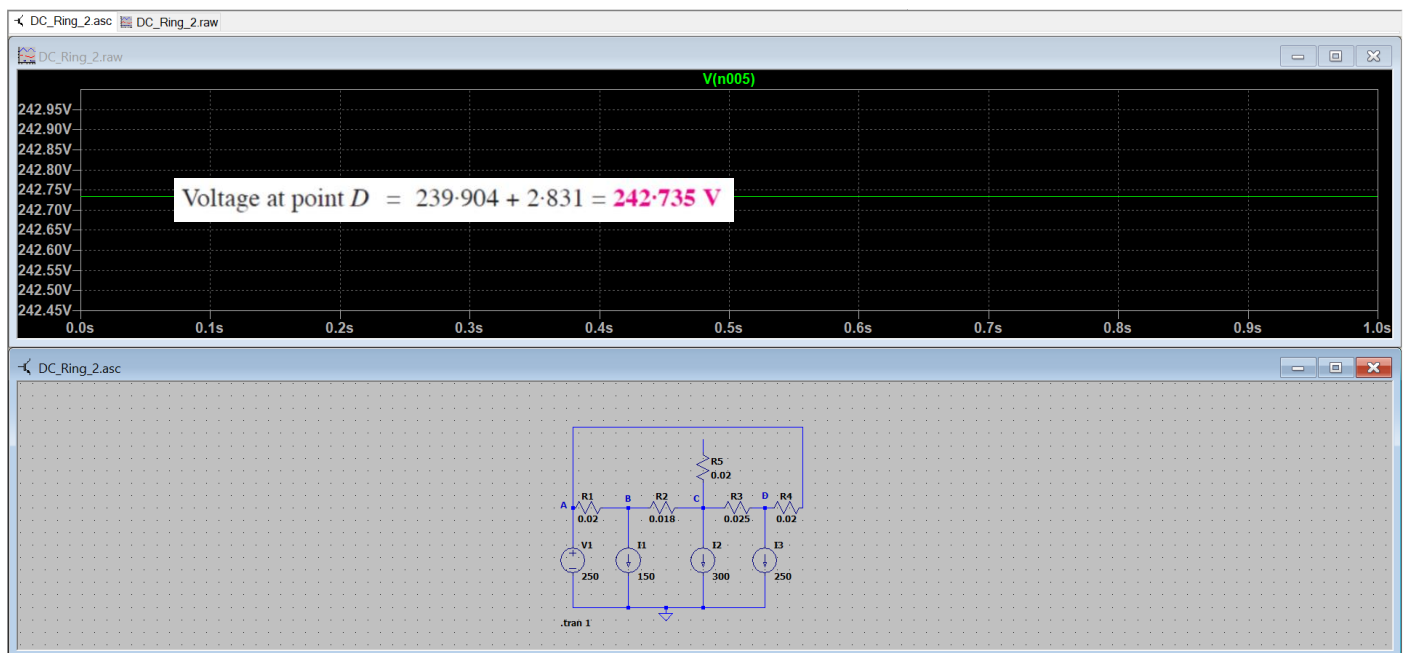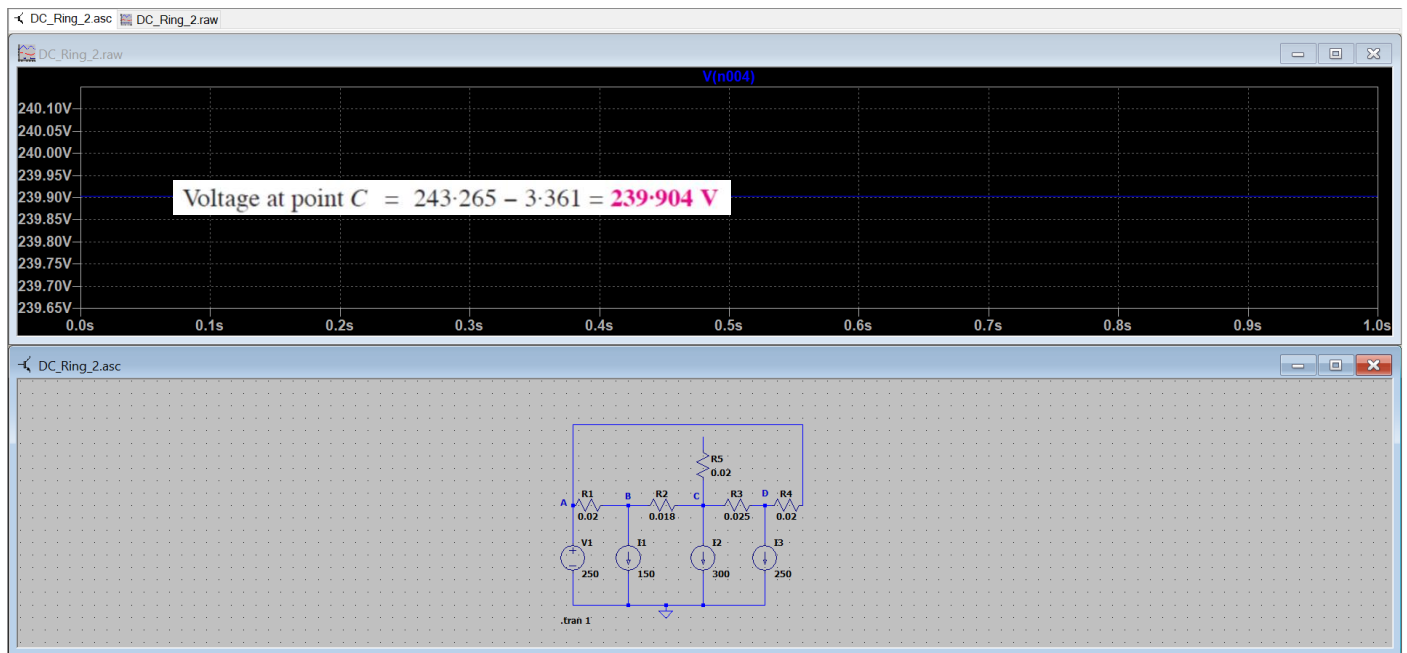


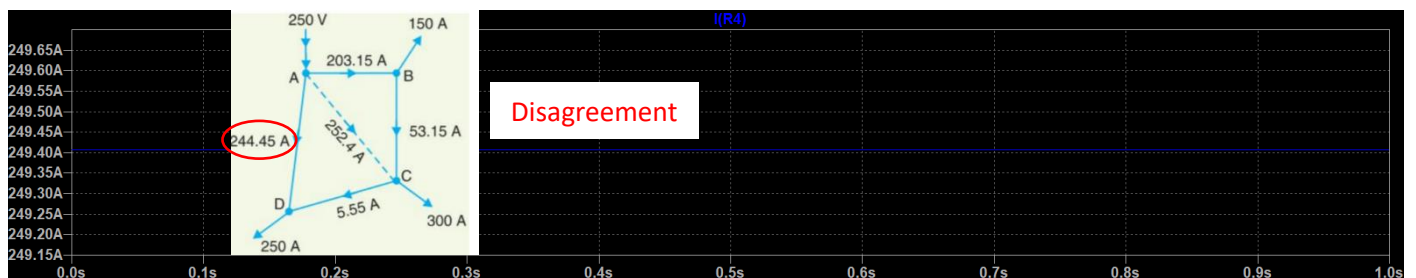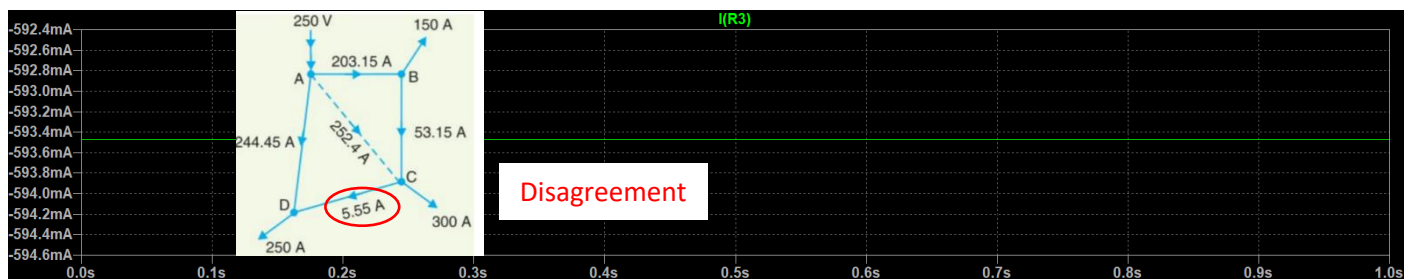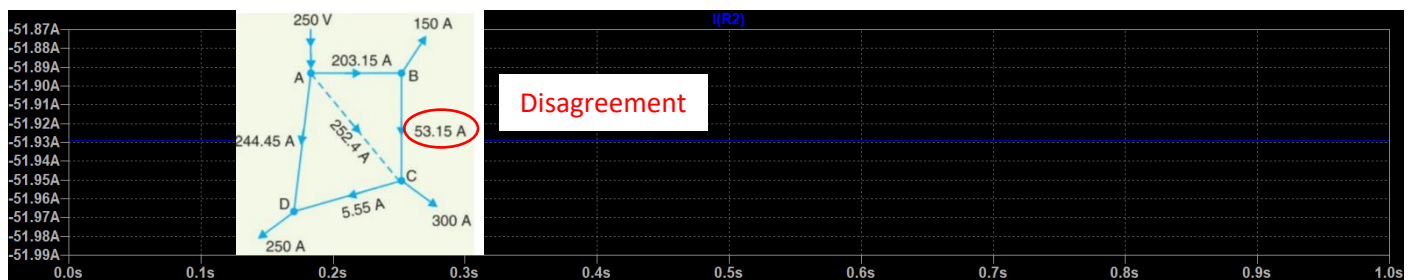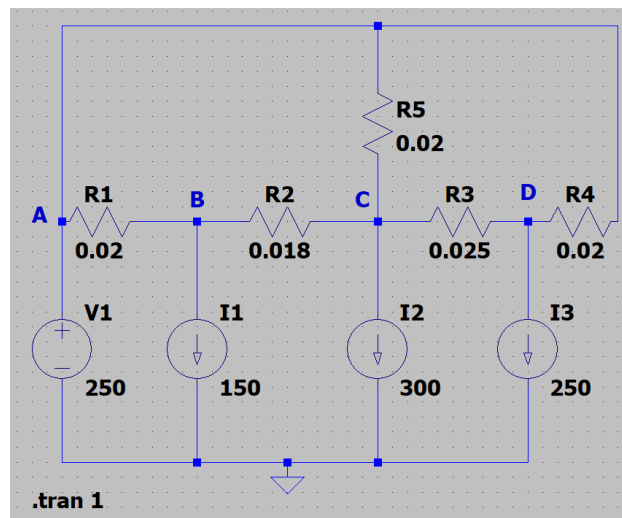

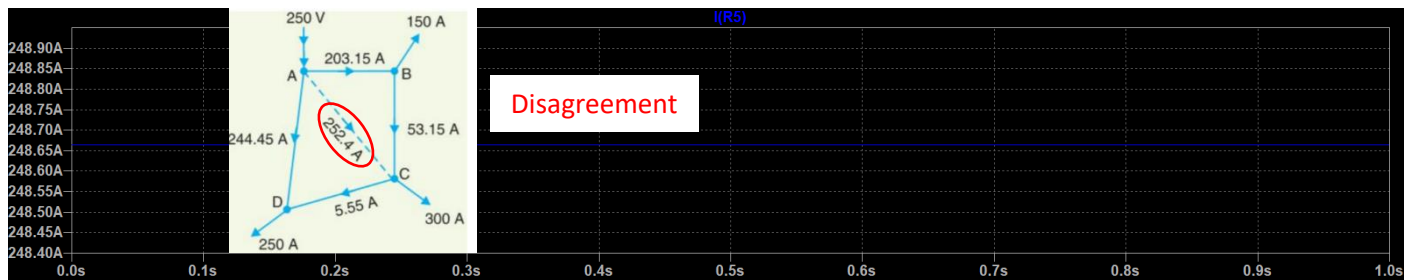

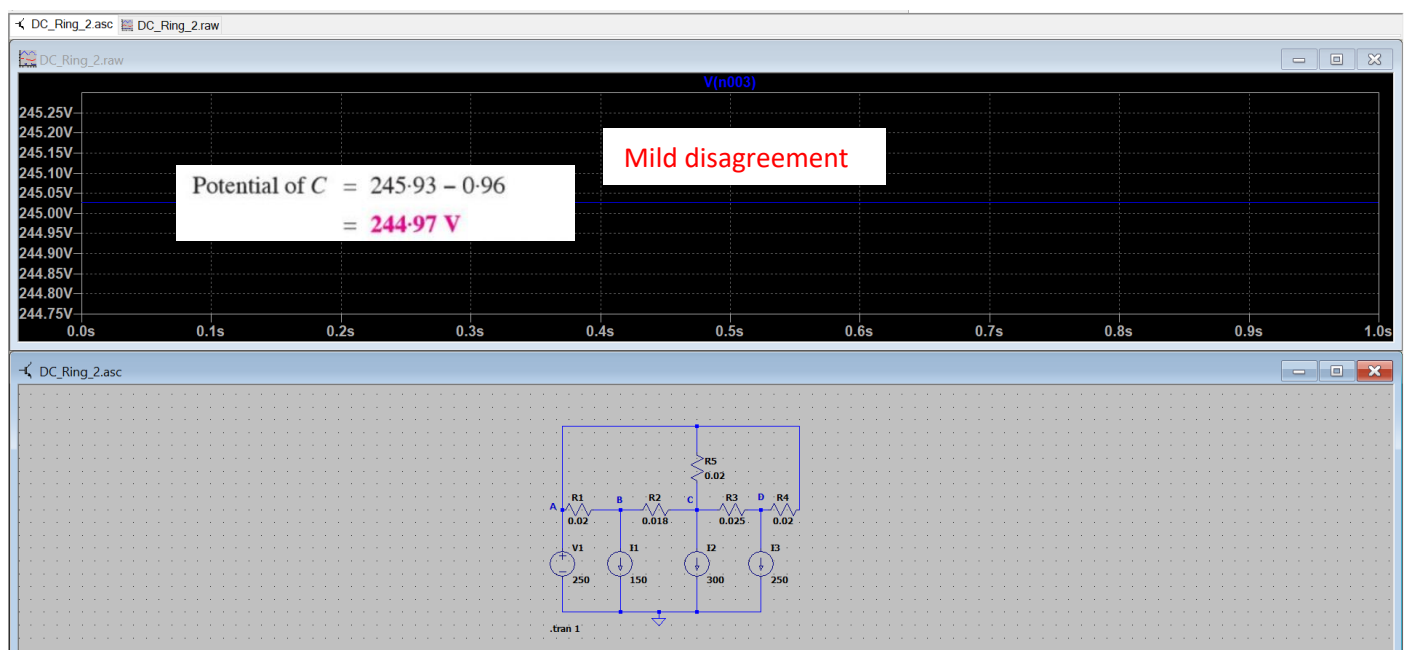
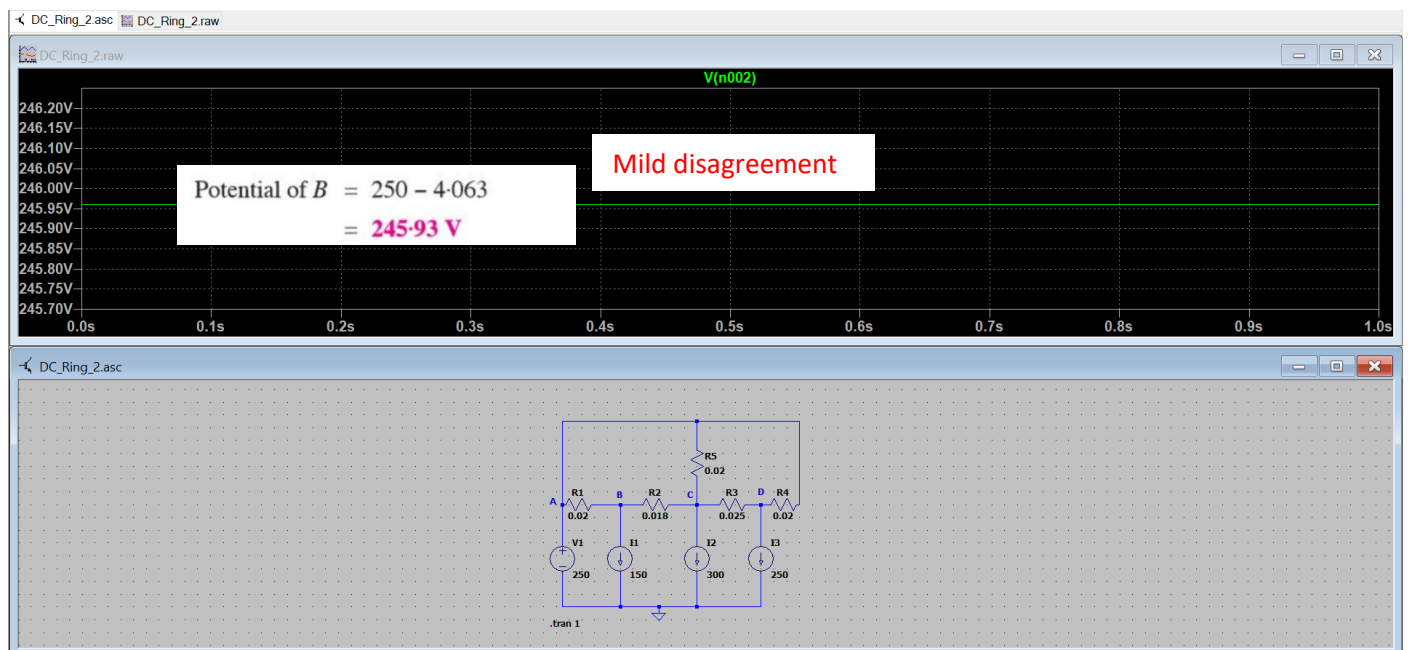
This task serves as a clear demonstration that more complex calculations can easily lead to errors when done manually. Therefore, it's advisable to promptly turn to simulations, especially considering their easy accessibility, to ensure accuracy in such cases.



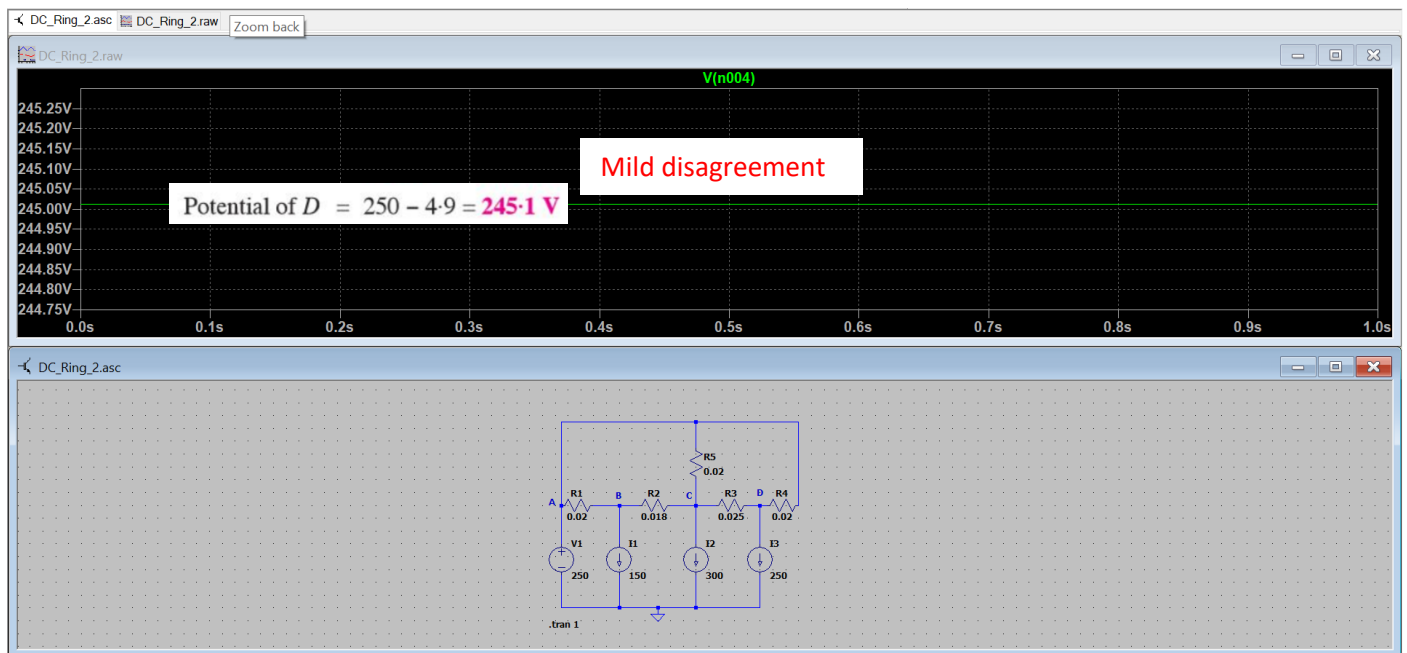

Try LTspice simulator at home for the following task:

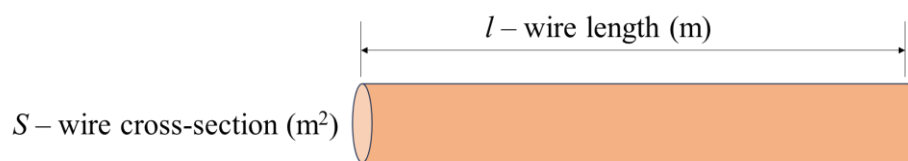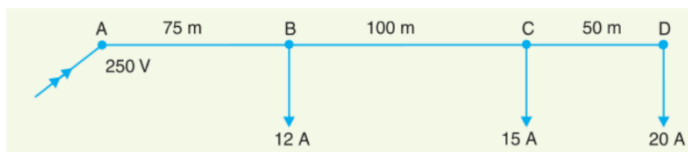The load distribution on a two-wire d.c. distributor is as shown below. The cross-sectional area of each conductor is 0.27 cm^2 . The end A is supplied at 250 V. Resistivity of the wire is $\rho = 1.78 \mu\Omega \text{ cm}$. Calculate (i) the current in each section of the conductor (ii) the two-core resistance of each section (iii) the voltage at each tapping point.



$$R_l = \rho \frac{l}{S} - \text{resistance of the wire } (\Omega)$$

$$\rho - \text{resistivity } (\Omega \times \text{m})$$

When calculating $R_l = \rho \frac{l}{S}$, transfer all units to the main SI units:

$$S = 0.27 \text{ cm}^2 \rightarrow S = 0.27 \times 0.01 \times 0.01 = 2.7 \times 10^{-5} \text{ m}^2 \text{ (1 cm = 0.01 m)}$$

$$\rho = 1.78 \mu\Omega \times \text{cm} \rightarrow \rho = 1.78 \times 10^{-6} \Omega \times 0.01 \text{ m} = 1.78 \times 10^{-8} \Omega \times \text{m (copper resistivity)}$$

$$R_l = \rho \frac{l}{S} = \frac{1.78 \times 10^{-8}}{2.7 \times 10^{-5}} \times l = \frac{1.78 \times 10^{-3}}{2.7} \times l \approx 6.66 \times 10^{-4} \times l \text{ (length in meters)}$$